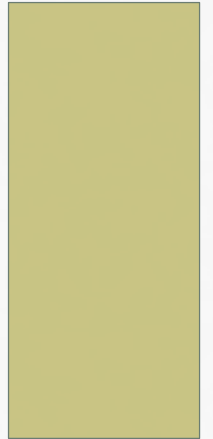



BASIC ELECTRONIC CIRCUITS

INSTITUTE CORE




INDEPENDENT SOURCES


- Voltage source

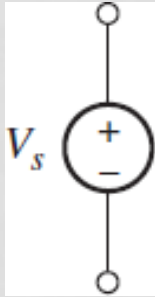

Dc voltage

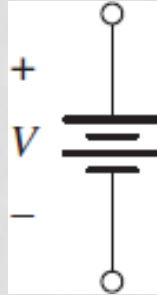


Battery

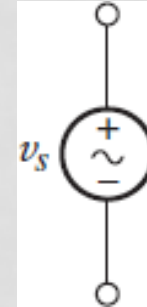


AC voltage

- Current Source

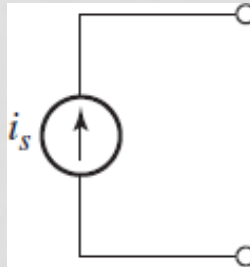


DEPENDENT SOURCES

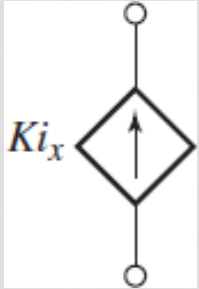


Current controlled current source


K is a dimensionless scaling factor

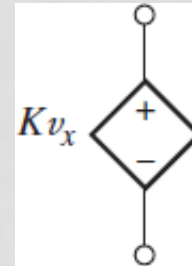

Voltage controlled voltage source

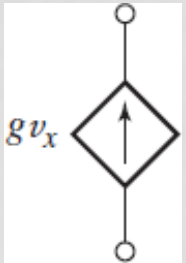

Voltage controlled current source

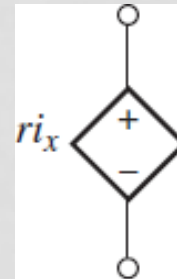


Current controlled voltage source

g , r are the scaling factor with units A/V and V/A respectively.


EXAMPLES

- If $v_2 = 3$ V, determine v_L .

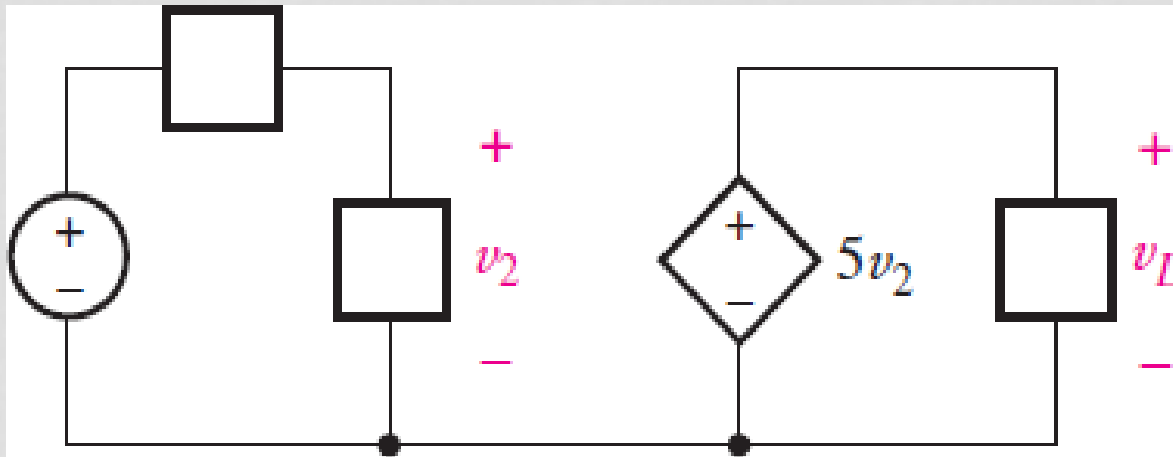

- Ans: $V_L = 15$ V.

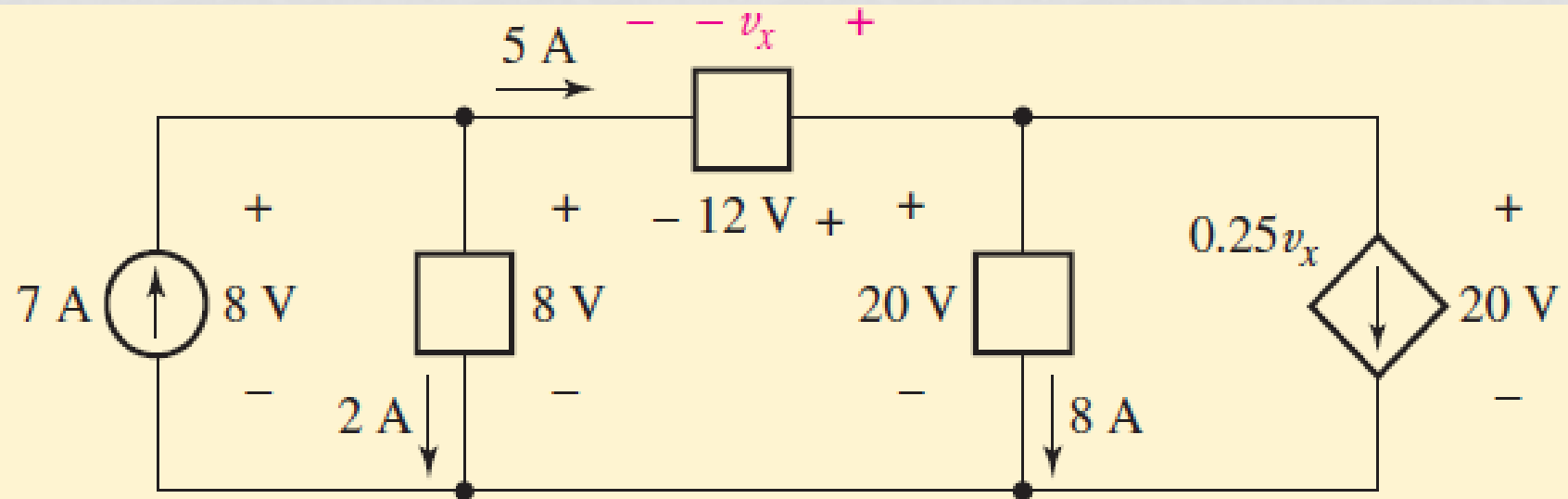
- Find the power absorbed by each element



Ans: (left to right) -56 W ; 16 W ; -60 W ; 160 W

OHM'S LAW

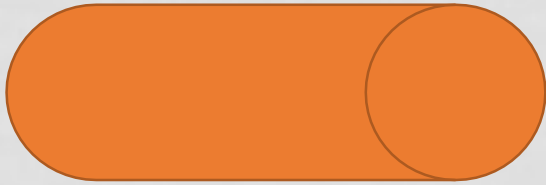- **Statement:** The voltage across “conducting” material is directly proportional to the current flowing through the material



Aluminium bar



Wooden bar

$$V = IR$$


Where : R – constant of proportionality,

Unit : Ohm (Ω)

- Power absorption, $P = VI = I^2R = V^2/R$

RESISTANCE AND RESISTIVITY

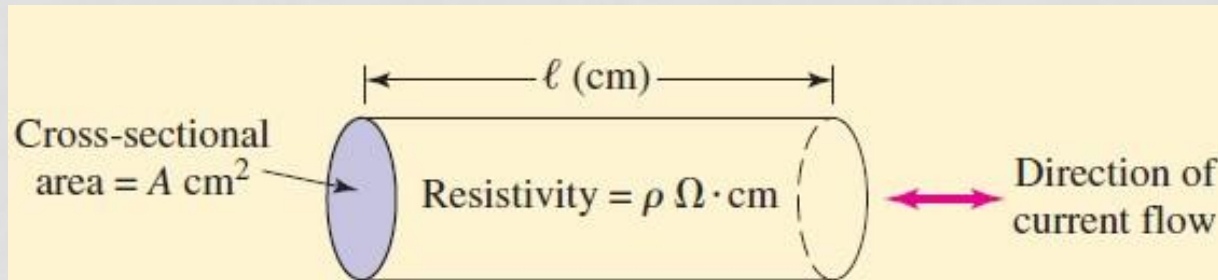- Resistance = Resistivity * length of the bar / Cross-sectional area of the bar




- $R = \rho \ell / A$
- Conductivity = $1/\text{resistivity}$; $\sigma = 1/\rho$

DEPENDENCY ON:

- Temperature: with increase in temp. resistivity increases.

$$R_t = R_0(1 + \alpha t)$$

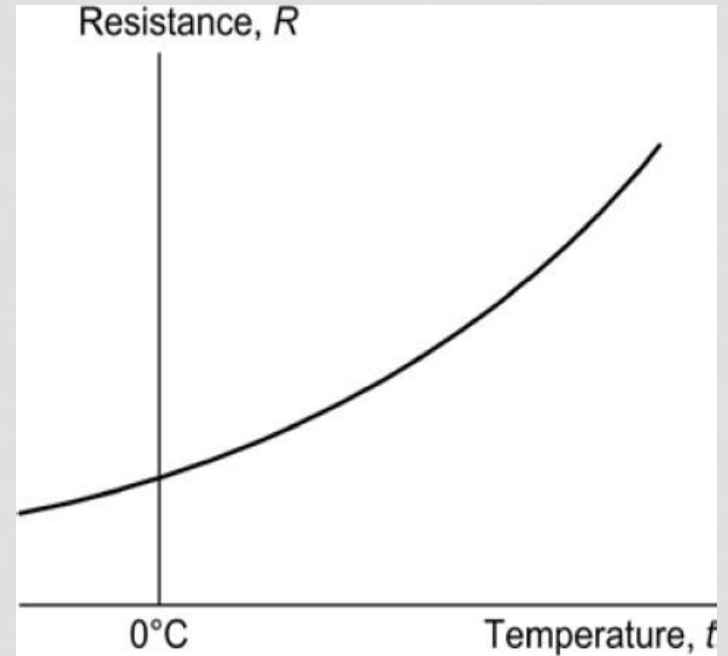
- α is called temperature coefficient ($/^{\circ}\text{C}$)
- Ex: A resistor has a temperature coefficient of $0.001 /^{\circ}\text{C}$. if the resistor has a resistance of $1.5 \text{ K}\Omega$ at 0°C , determine the resistance at 80°C ?



KIRCHHOFF'S LAWS: KCL


- Algebraic sum of currents entering the node is zero.

$$\sum_{n=1}^N i_n = 0$$

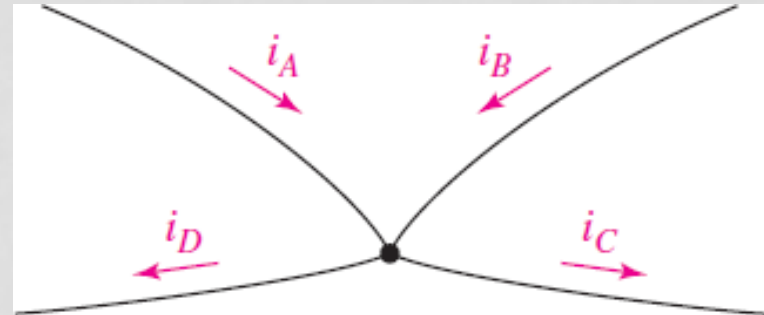


$$i_A + i_B + (-i_C) + (-i_D) = 0$$

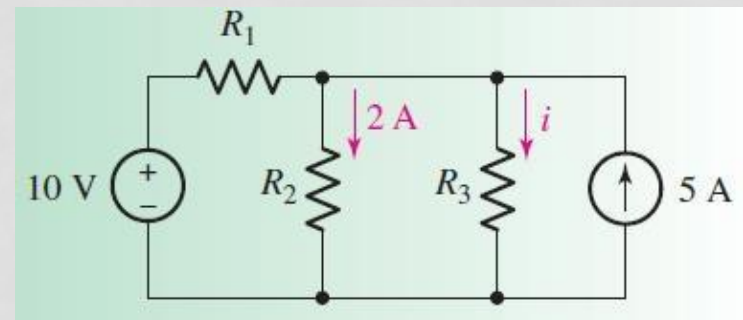- Ex 1: if the voltage source produces a current 3A, determine i ?



KVL

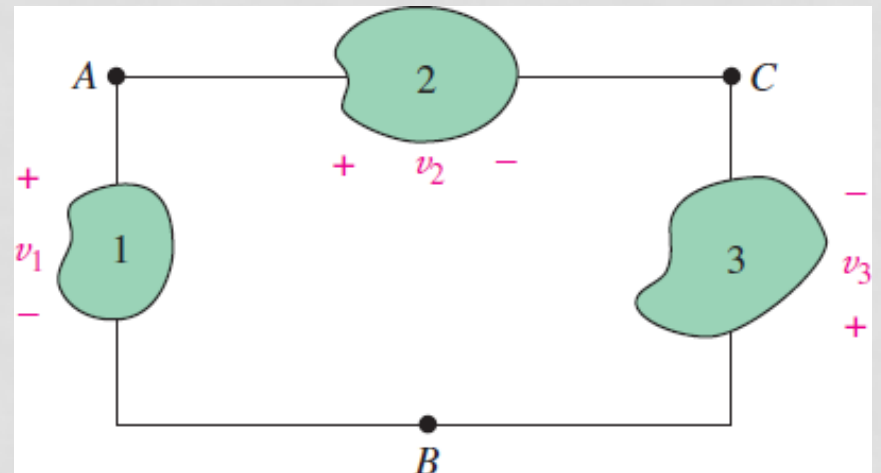


- The algebraic sum of voltages around any closed path is zero.



$$\sum_{n=1}^N v_n = 0$$

$$-v_1 + v_2 - v_3 = 0$$

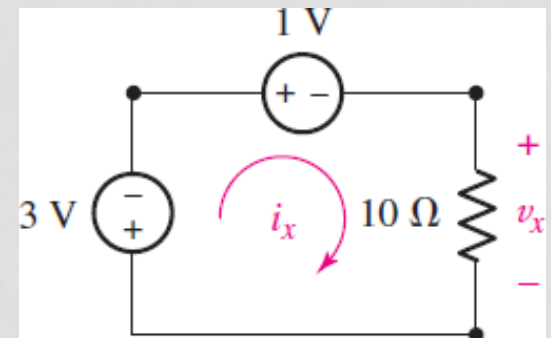
- Ex 2: Determine v_x and i_x
- Ans: $v_x = -4$ V and $i_x = -400$ mV.



SERIES AND PARALLEL CONNECTED SOURCES

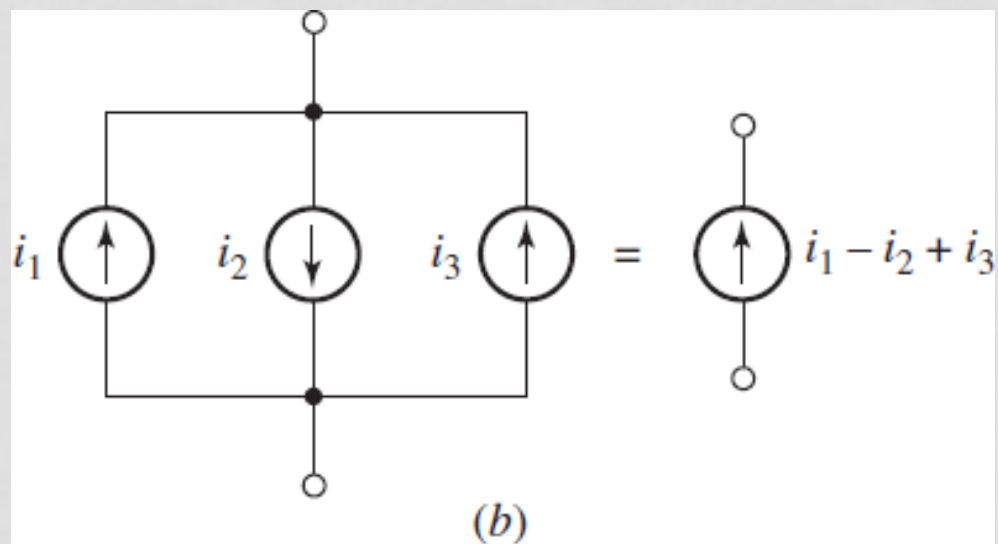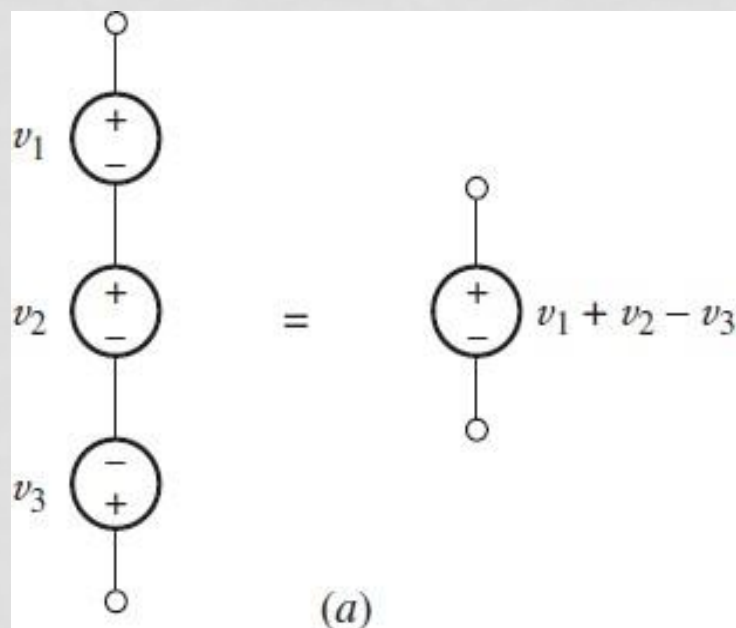

RESISTORS IN SERIES

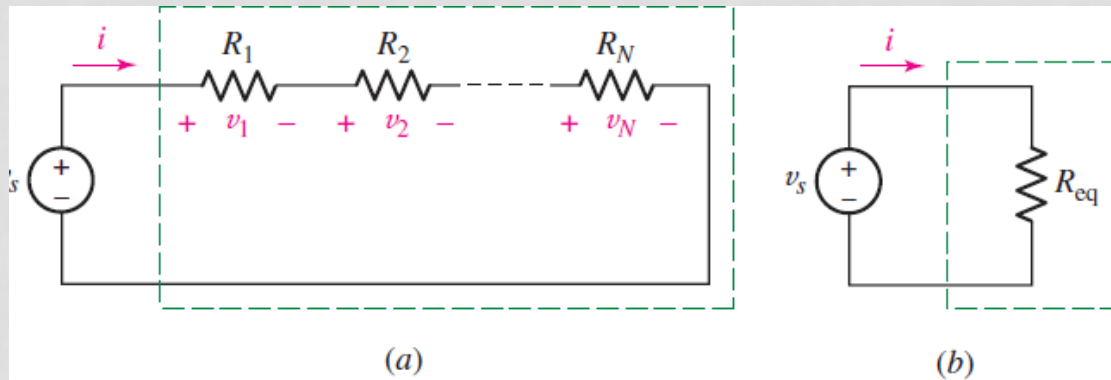

$$v_s = R_1 i + R_2 i + \cdots + R_N i = (R_1 + R_2 + \cdots + R_N) i$$

$$v_s = R_{eq} i$$

$$R_{eq} = R_1 + R_2 + \cdots + R_N$$


RESISTORS IN PARALLEL

$$i_s = i_1 + i_2 + \cdots + i_N$$


$$i_s = \frac{v}{R_1} + \frac{v}{R_2} + \cdots + \frac{v}{R_N}$$

$$= \frac{v}{R_{\text{eq}}}$$
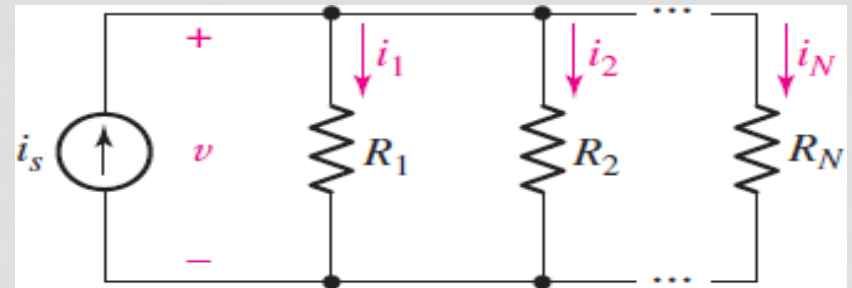
$$\frac{1}{R_{\text{eq}}} = \frac{1}{R_1} + \frac{1}{R_2} + \cdots + \frac{1}{R_N}$$



(a)

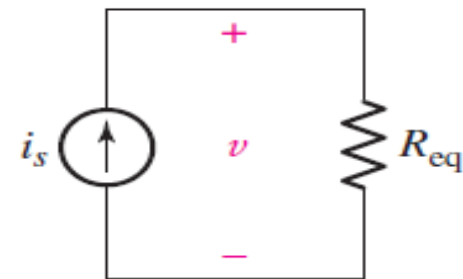


(b)

VOLTAGE DIVISION

$$v = v_1 + v_2 = iR_1 + iR_2 = i(R_1 + R_2)$$

$$i = \frac{v}{R_1 + R_2}$$

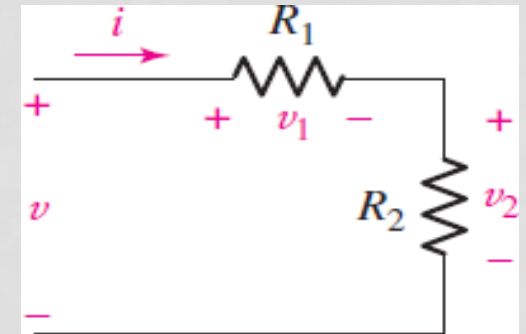

$$v_1 = \frac{R_1}{R_1 + R_2} v \quad v_2 = \frac{R_2}{R_1 + R_2} v$$

$$v_k = \frac{R_k}{R_1 + R_2 + \dots + R_N} v$$


Current division

$$i_2 = \frac{v}{R_2} = \frac{i(R_1 \parallel R_2)}{R_2} = \frac{i}{R_2} \frac{R_1 R_2}{R_1 + R_2}$$

$$i_2 = i \frac{R_1}{R_1 + R_2}$$

$$i_1 = i \frac{R_2}{R_1 + R_2}$$
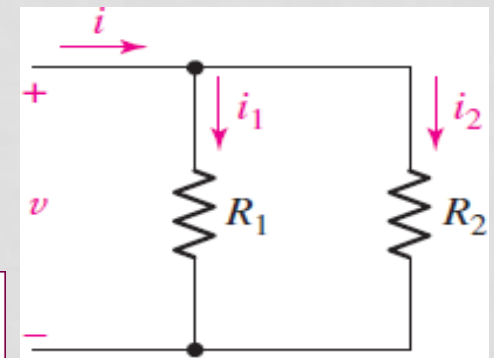
$$i_k = i \frac{\frac{1}{R_k}}{\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N}}$$



THANK YOU