
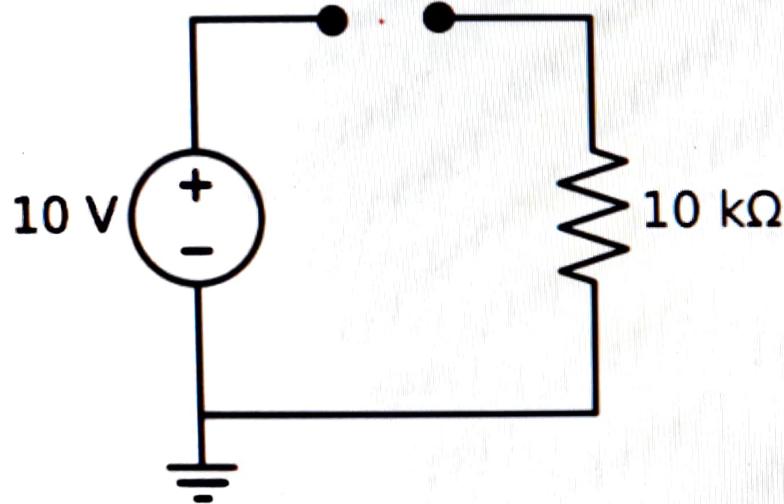


Resistor circuit

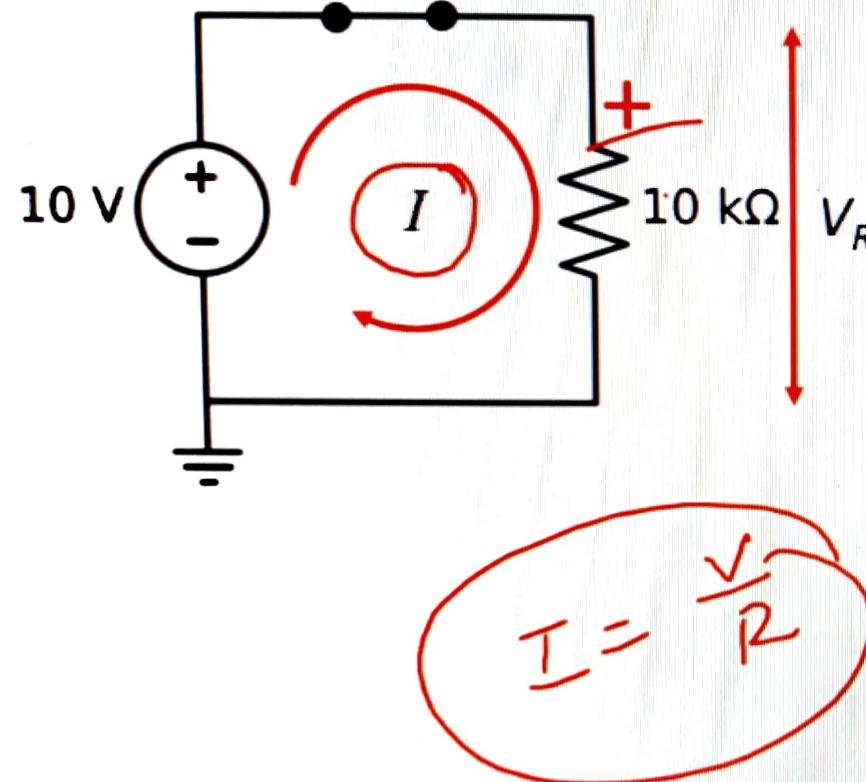

Open circuit, current = 0 A

Resistor circuit



Open circuit, current = 0 A

Closed circuit, current = I A

1

What is the magnitude of current

SAMYAK
1mA

JAYANTH
V/R

SHUBHAM
1mA

Circuit laws

- **Kirchhoff's current law (KCL)**
 - Algebraic sum of currents at a junction is zero
 - Algebraic sum of currents entering a junction is equal to the algebraic sum of currents leaving the junction
- **Kirchhoff's voltage law (KVL)**
 - Algebraic sum of voltages in a closed loop is equal to zero
 - Algebraic sum of potential rise is equal to algebraic sum of potential drops


Kirchhoff's current law (KCL)

Algebraic sum of currents at a junction is zero

$$I_1 - I_2 + I_3 - I_4 = 0$$

$$I_1 + I_3 = I_2 + I_4$$

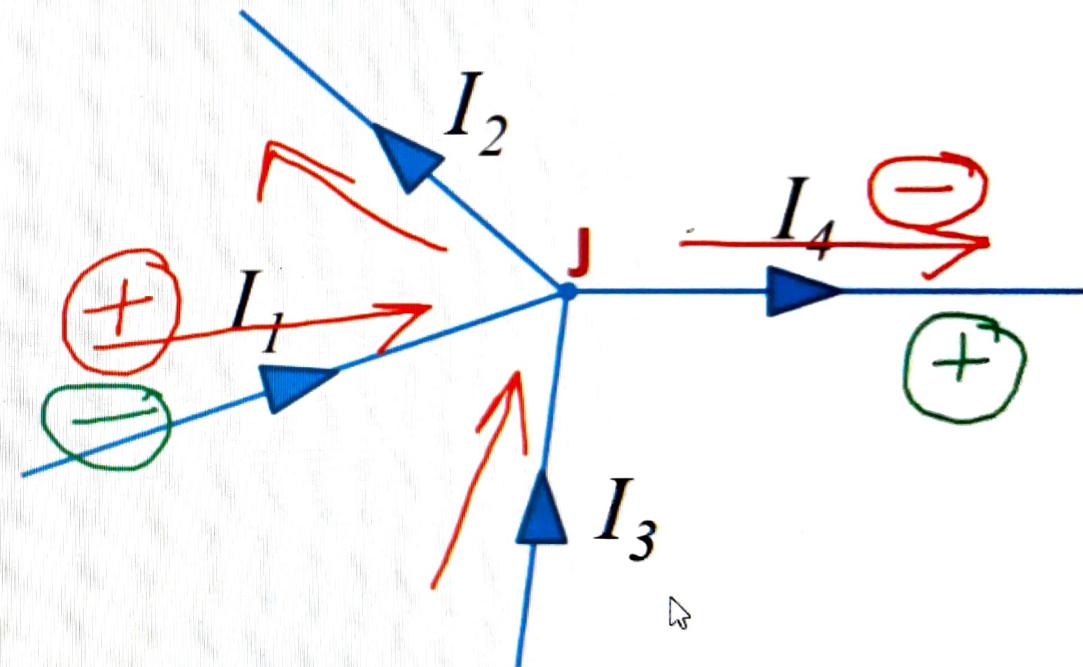Sum of currents entering a junction is equal to the sum of currents leaving the junction




Kirchhoff's voltage law (KVL)

Algebraic sum of voltages in a closed loop is equal to zero

$$-V + V_{R_1} + V_{R_2} + V_{R_3} + V_{R_4} = 0$$
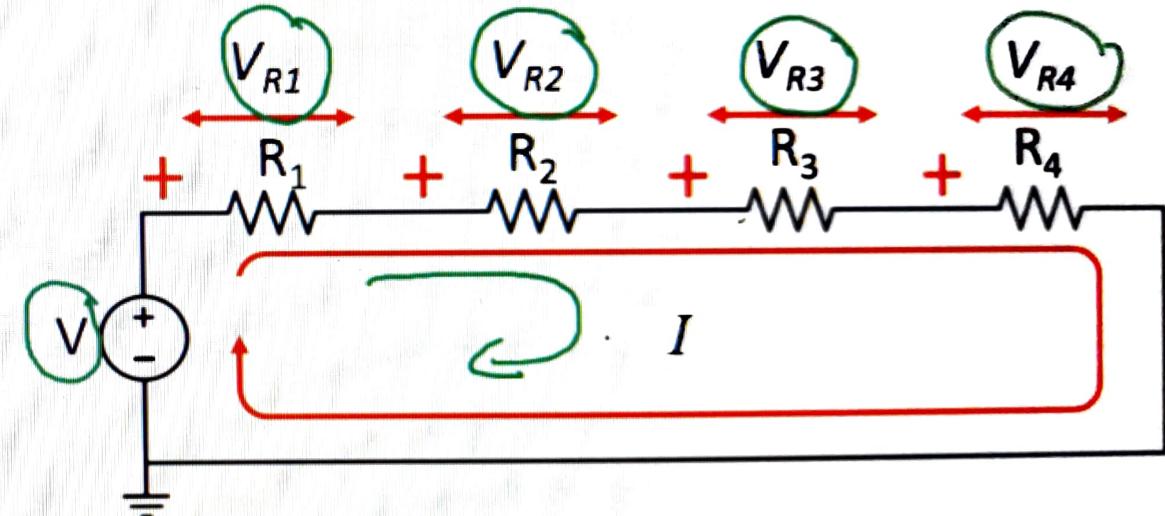
$$V = V_{R_1} + V_{R_2} + V_{R_3} + V_{R_4}$$



R circuit: what is the current flowing?

KVL

$$-V_S + IR = 0$$

$$V_S = IR$$

$$10 = I(10k)$$

$$I = \frac{10}{10k} = 1\text{mA}$$

Voltage drop across $10\text{k}\Omega$ resistor


$$V_R = IR$$

$$V_R = (1\text{m})(10\text{k}) = 10\text{V}$$

$$V_S = V_R$$



KVL

I and V_R are unknown variables

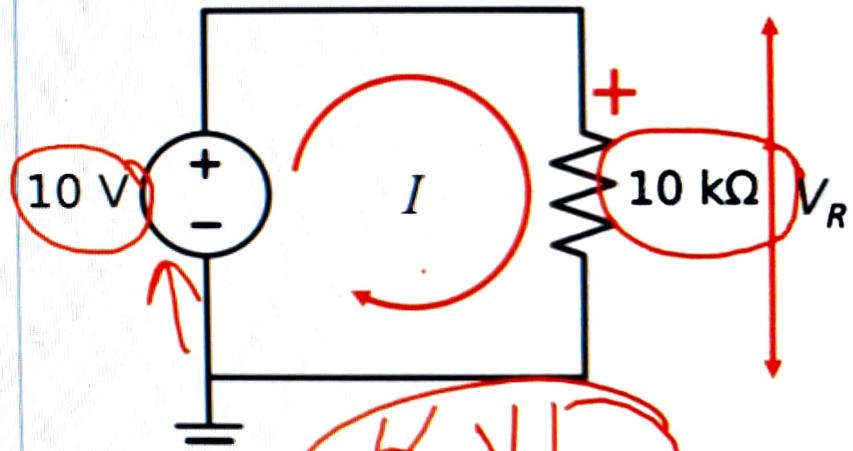


Scientific notation
 $\frac{10}{10 \times 10^3} = 0.0000$
 $= 1\text{mA}$

Series R circuit

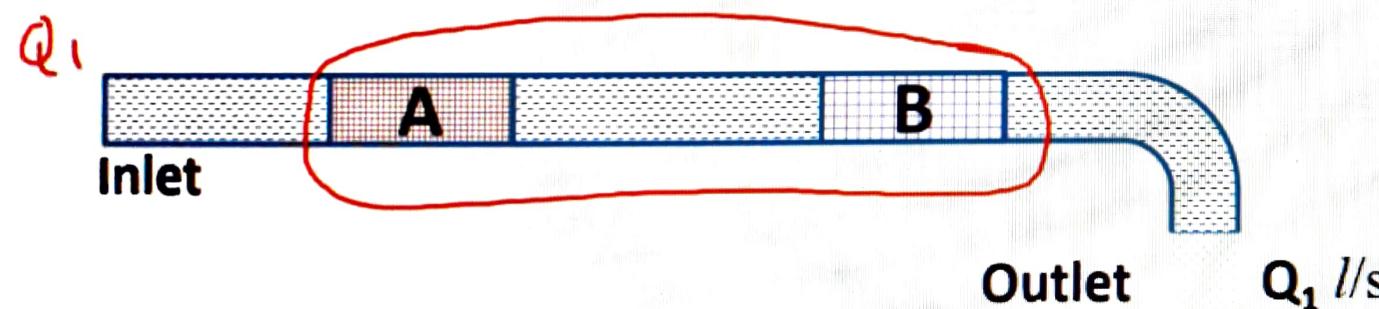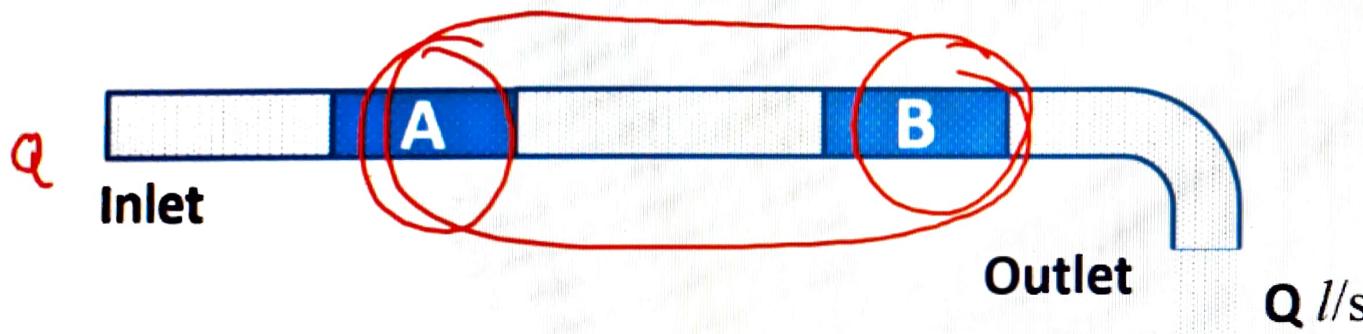


Fluid flow is equal at inlet and outlet

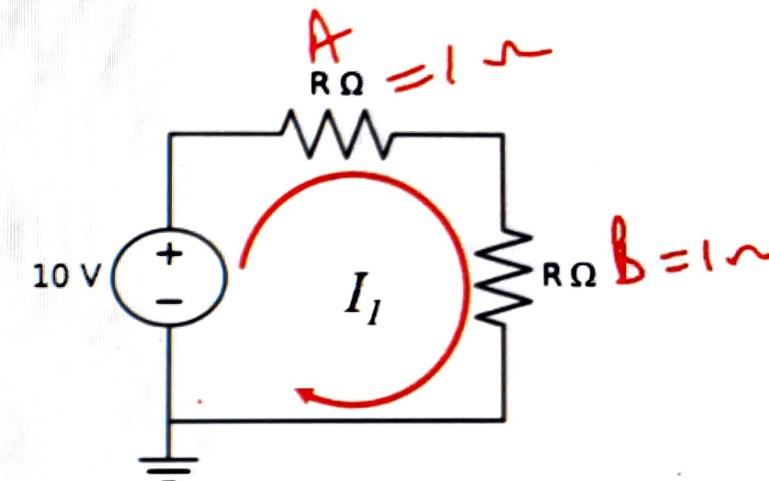Same current flows in
series circuit elements



Equal resistors

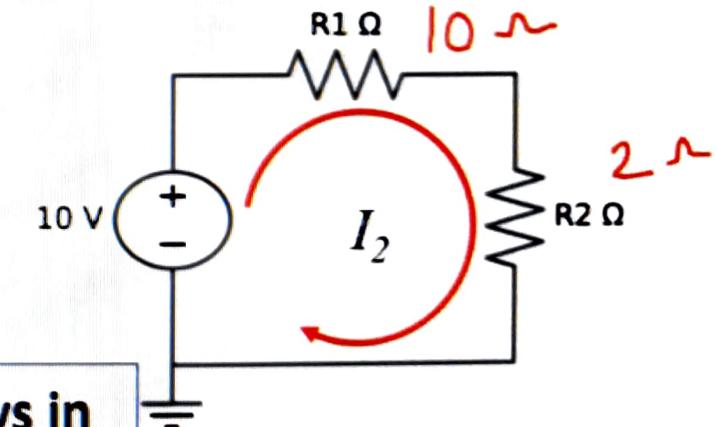

Unequal resistors

Series R circuit: Equal resistors

KVL

$$-V_s + V_{R_1} + V_{R_2} = 0$$

$$-V_s + IR_1 + IR_2 = 0$$

$$V_s = IR_1 + IR_2$$

$$V_s = I(R_1 + R_2)$$

$$10 = I(10\text{k}+10\text{k})$$

$$I = \frac{10}{10\text{k}+10\text{k}} = 0.5\text{mA}$$

Current is flowing in
CW direction


Voltage drop across resistors

$$V_{R_1} = IR_1$$

$$V_{R_1} = (0.5\text{m})(10\text{k}) = 5\text{V}$$

$$V_{R_2} = IR_2$$
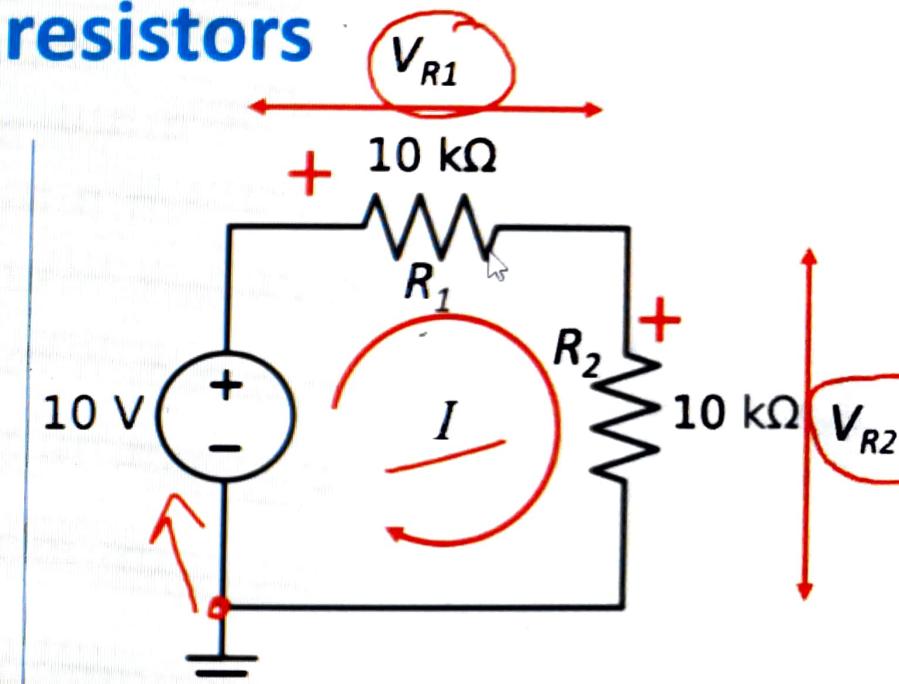
$$V_{R_2} = (0.5\text{m})(10\text{k}) = 5\text{V}$$



unknown variables
 I , V_{R_1} and V_{R_2}

Series R circuit: Different value resistors

$$I = 0.1 \text{ mA}$$

Let us calculate voltage drops


$$V_{R_1} = IR_1 = (0.1 \text{ m})(10 \text{ k}) = 1 \text{ V}$$

$$V_{R_2} = IR_2 = (0.1 \text{ m})(20 \text{ k}) = 2 \text{ V}$$

$$V_{R_3} = IR_3 = (0.1 \text{ m})(30 \text{ k}) = 3 \text{ V}$$

$$V_{R_4} = IR_4 = (0.1 \text{ m})(40 \text{ k}) = 4 \text{ V}$$

$$\underline{\underline{10 \text{ V}}}$$

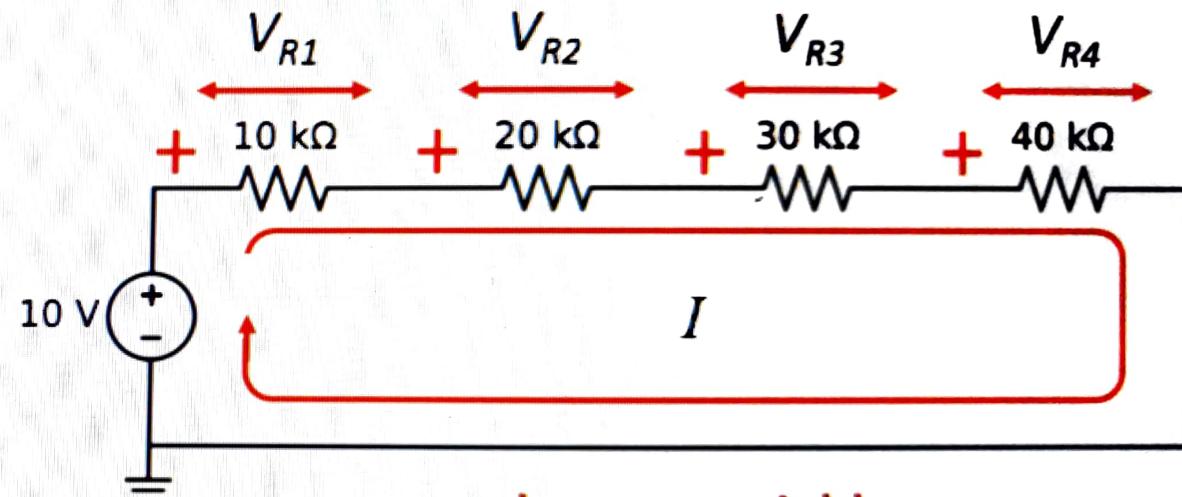

unknown variables
 I , V_{R1} , V_{R2} , V_{R3} and V_{R4}

RAHUL

1V,2V,3V,4V

CHAND

Series R circuit: Different value resistors

KVL to the loop

$$V_s = V_{R_1} + V_{R_2} + V_{R_3} + V_{R_4} \rightarrow (1)$$


$$V_s = I(R_1 + R_2 + R_3 + R_4)$$

$$V_s = I(R_{eq})$$

$$I = \frac{V_s}{R_1 + R_2 + R_3 + R_4}$$

$$I = \frac{10}{10k + 20k + 30k + 40k}$$

$$I = 0.1 \text{ mA}$$

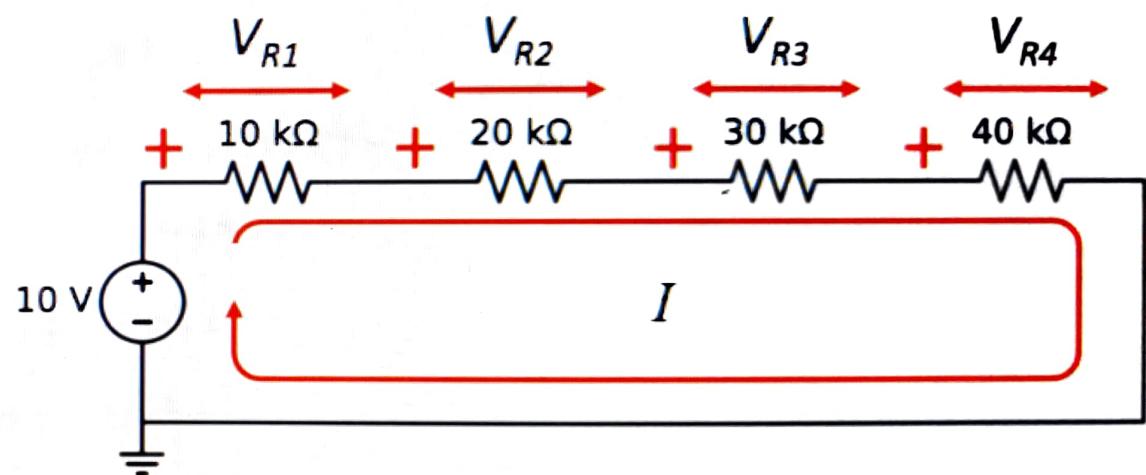


unknown variables
 I , V_{R1} , V_{R2} , V_{R3} and V_{R4}

Series R circuit: Points to remember




Current is same in all the elements

Voltage drop is in proportion to the magnitude of resistance

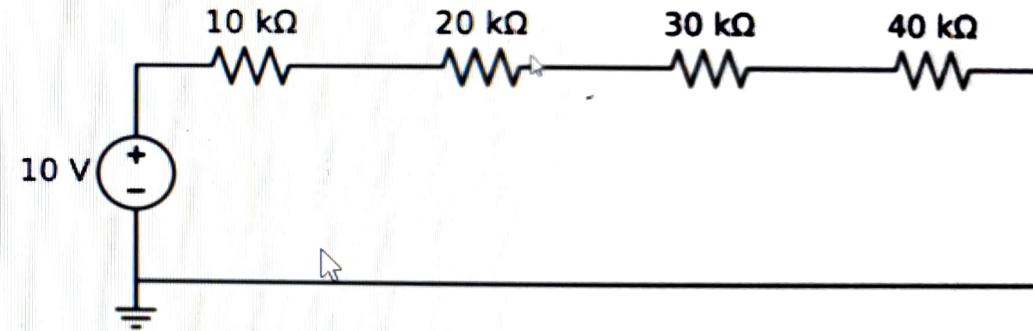Voltage rise = Sum of Voltage drops in all the elements




Parallel R circuit

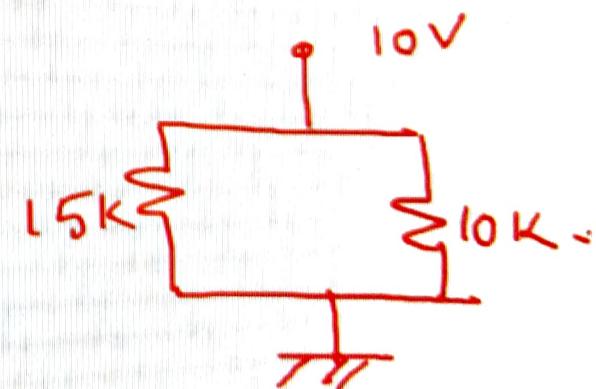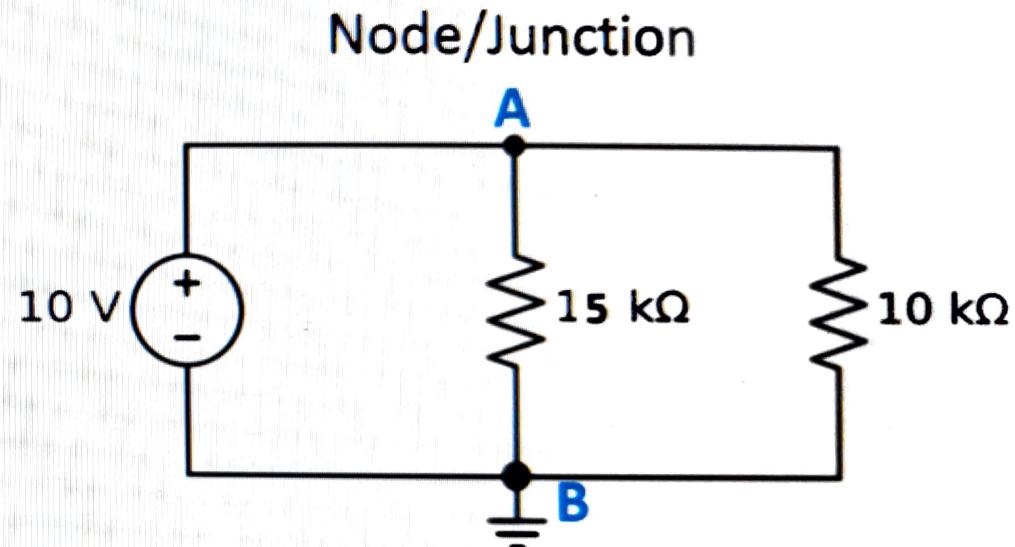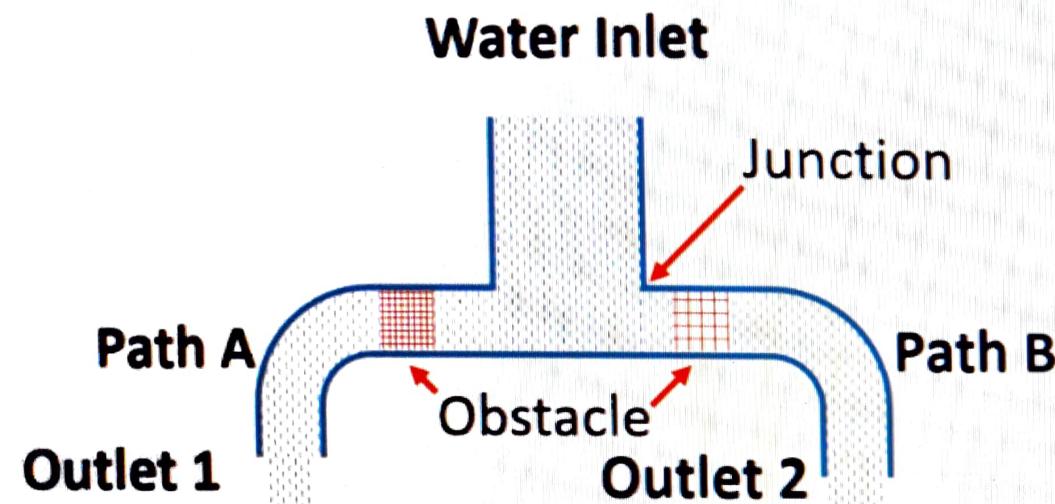


Parallel R circuit

$$I_1 < I_2$$

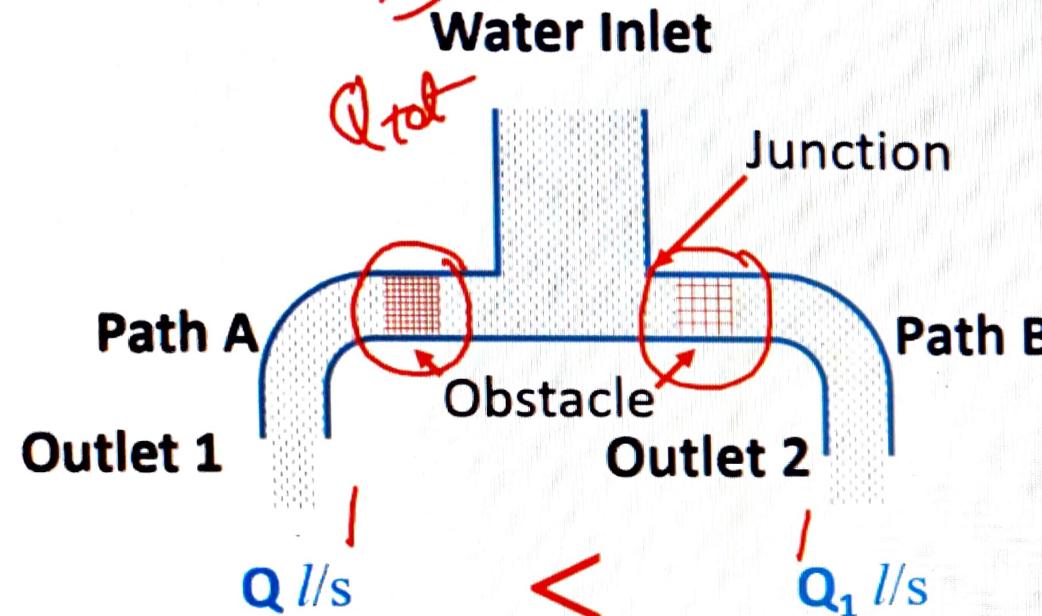


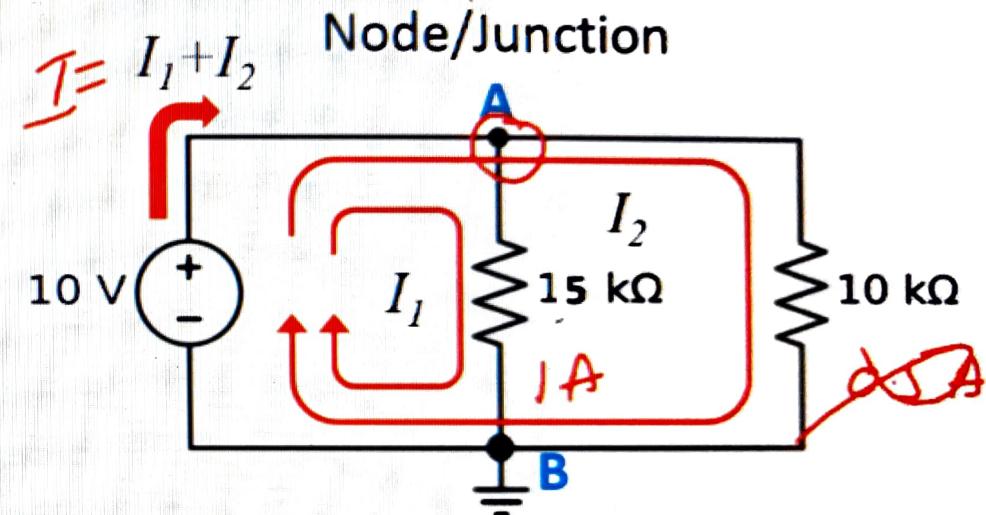- Water divides at a junction
- More water flows out of outlet, if the obstruction is less



- I_1 I_2 current
- Current divides at a junction
 - Magnitude of current is less if resistance is more

Series resistive circuit

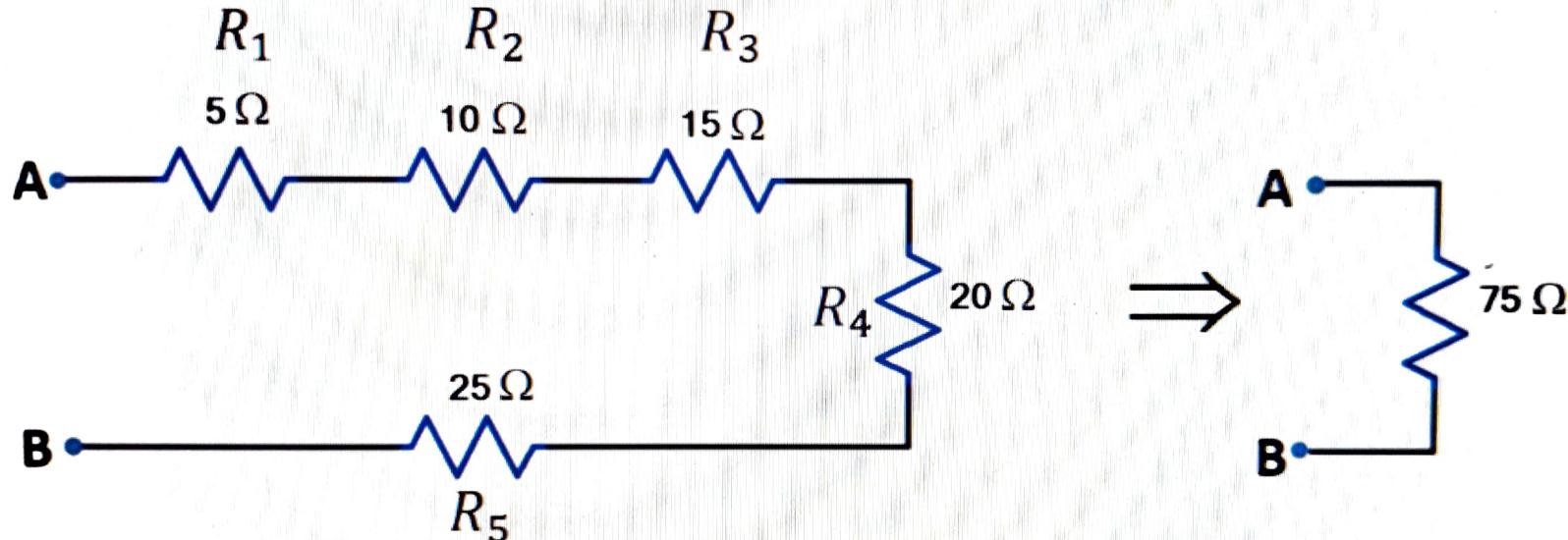


$$R_{eq} = R_1 + R_2 + R_3 + \dots + R_n$$

$$R_{eq} = 5 + 10 + 15 + 20 + 25 = 75\ \Omega$$

Equivalent resistance is greater than the largest resistance value.

Parallel resistive circuit

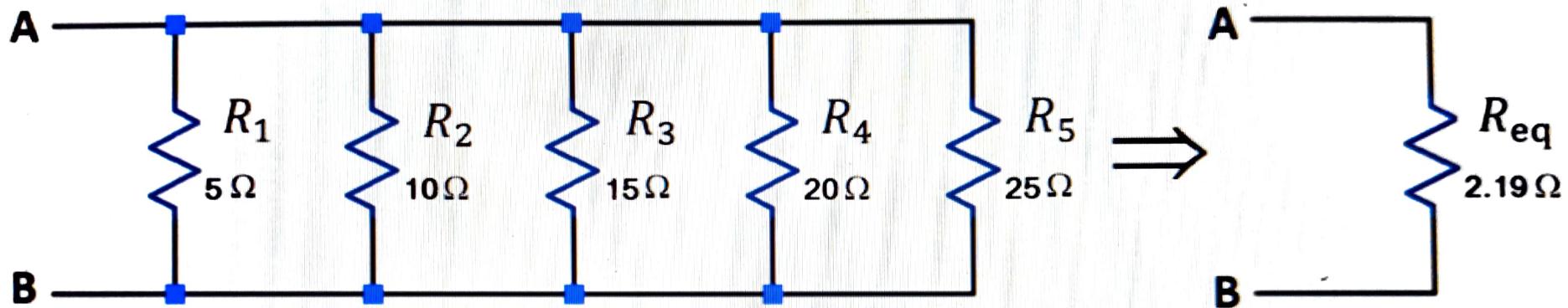


$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_5}$$

$$\frac{1}{R_{eq}} = \frac{1}{5} + \frac{1}{10} + \frac{1}{15} + \frac{1}{20} + \frac{1}{25}$$

$$R_{eq} = 2.19\Omega$$

Equivalent resistance is lesser than the smallest resistance value.

Series-Parallel resistive circuit

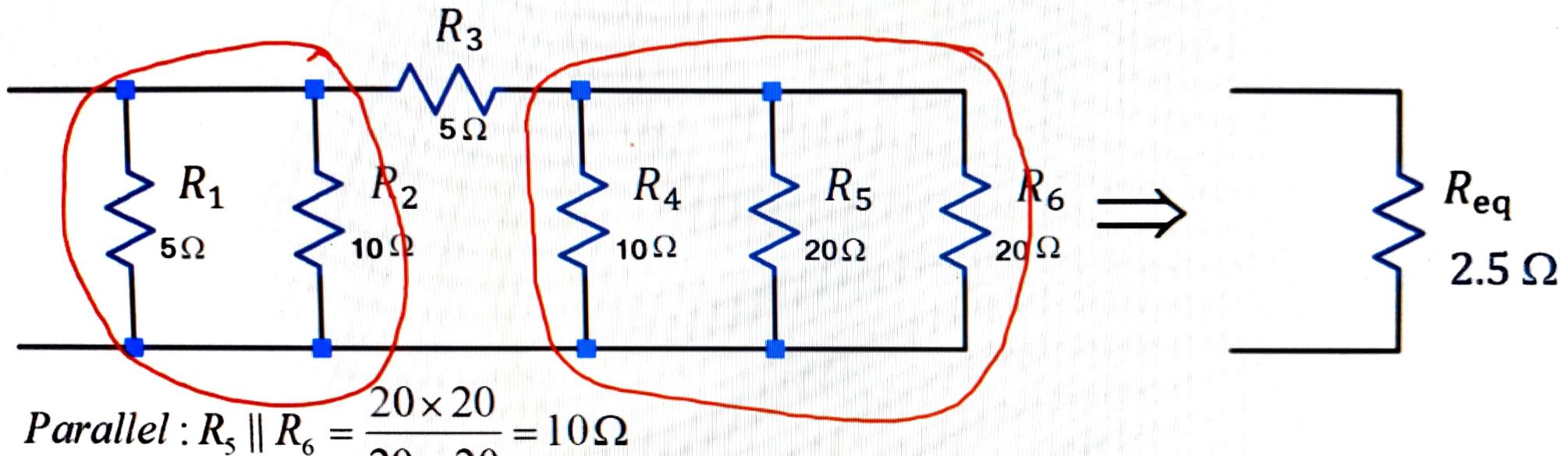


Parallel : $10\Omega \parallel R_4 = 5\Omega$

Series : $5\Omega + R_3 = 10\Omega$

Parallel : $10\Omega \parallel R_2 = 5\Omega$

Parallel : $5\Omega \parallel R_1 = 2.5\Omega$

Series-Parallel resistive circuit

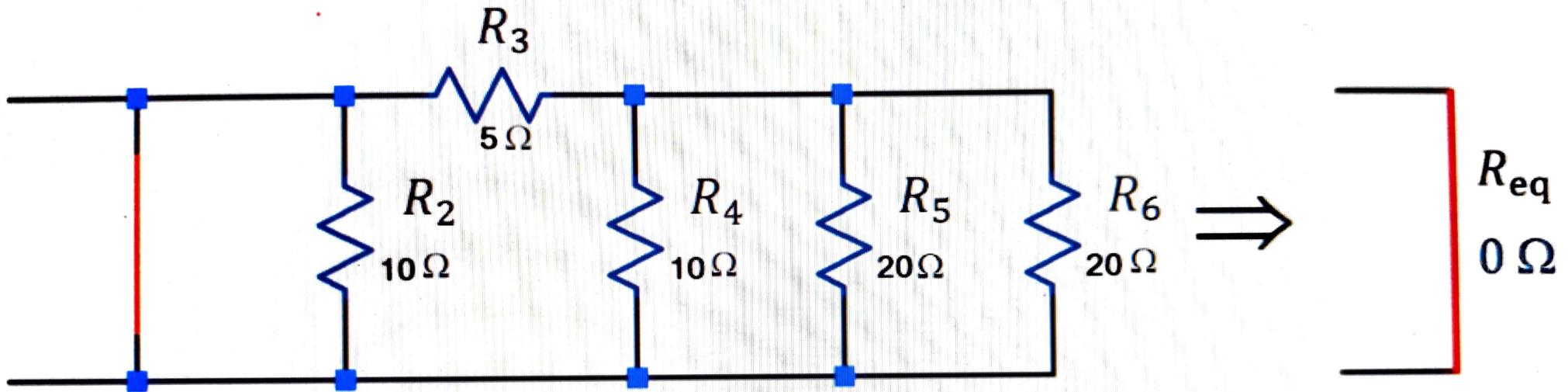

$$\text{Parallel : } R_5 \parallel R_6 = \frac{20 \times 20}{20 + 20} = 10\Omega$$


$$\text{Parallel : } 10\Omega \parallel R_4 = 5\Omega$$

$$\text{Series : } 5\Omega + R_3 = 10\Omega$$

$$\text{Parallel : } 10\Omega \parallel R_2 = 5\Omega$$

$$\text{Parallel : } 5\Omega \parallel 0\Omega = 0\Omega$$


Series-Parallel resistive circuit

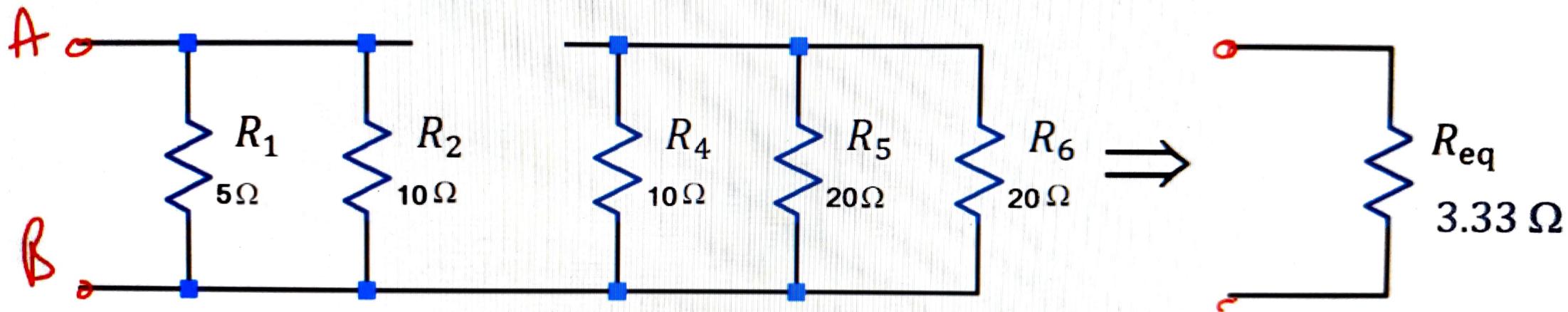

$$\text{Parallel : } R_1 \parallel R_2 = \frac{10 \times 5}{10 + 5} = 3.33\ \Omega$$


Problem: Equivalent resistance

$$\frac{10 \times 15}{25}$$


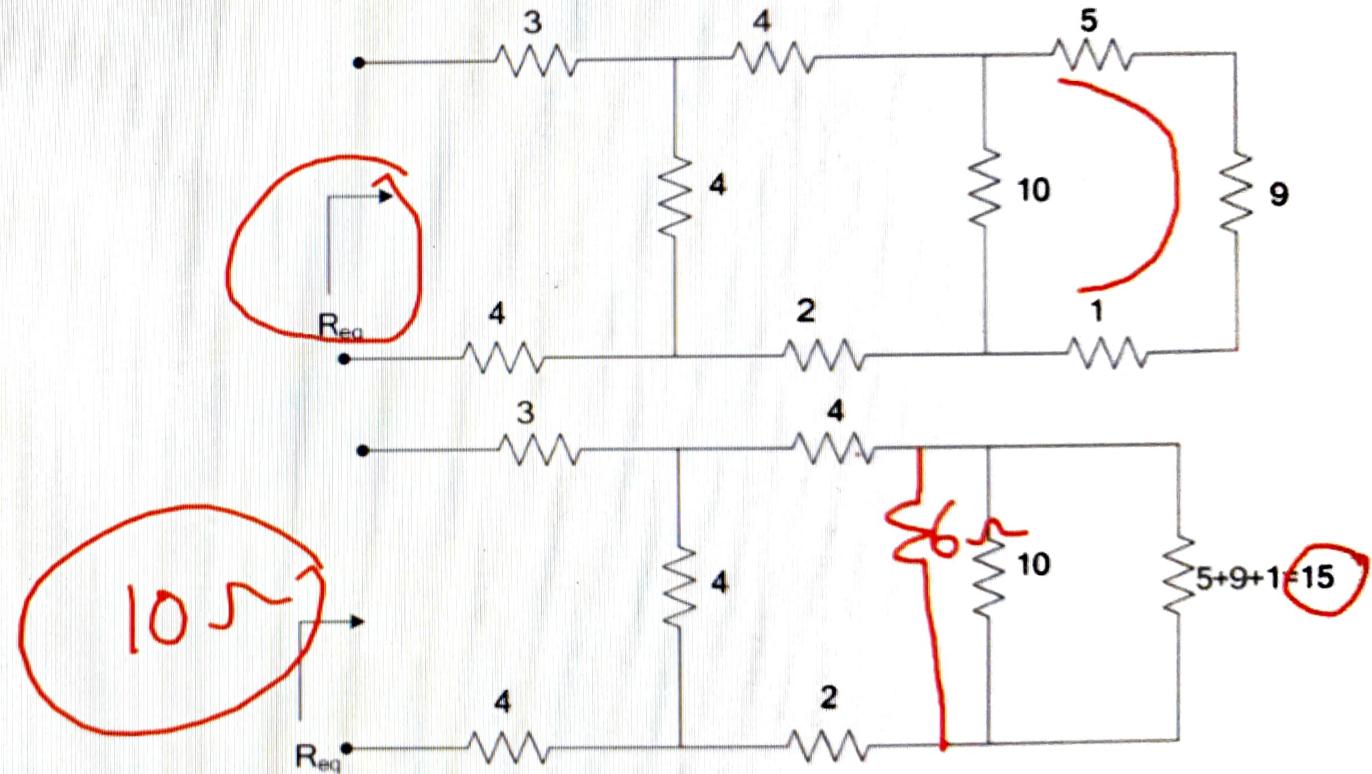


Problem: Equivalent resistance

- Between A & B and C & D terminals

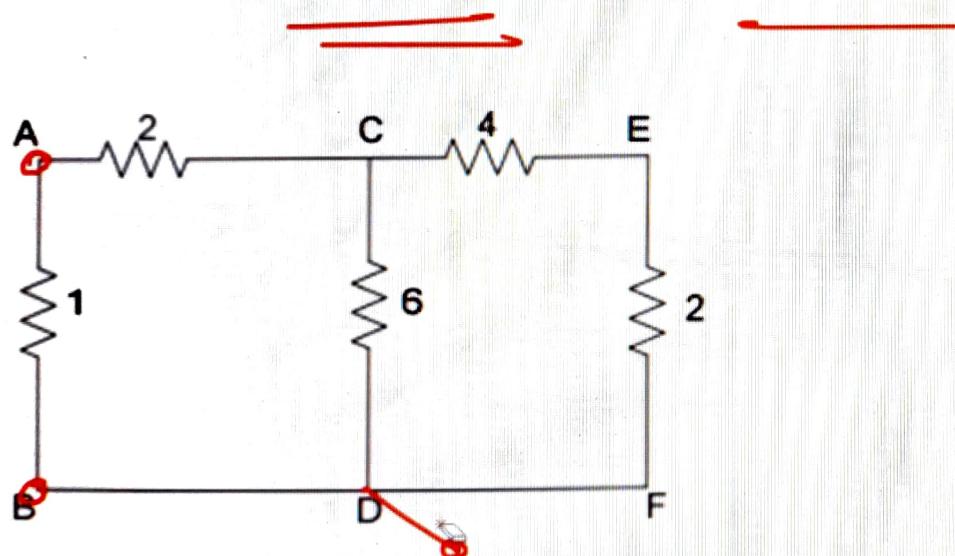


Between A & B


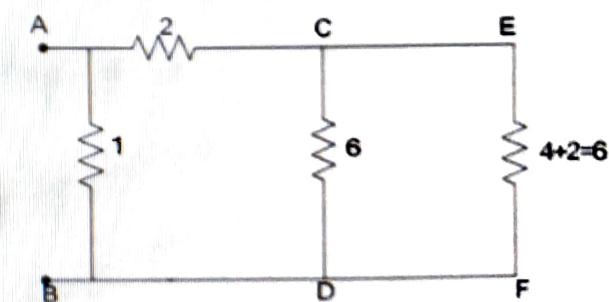
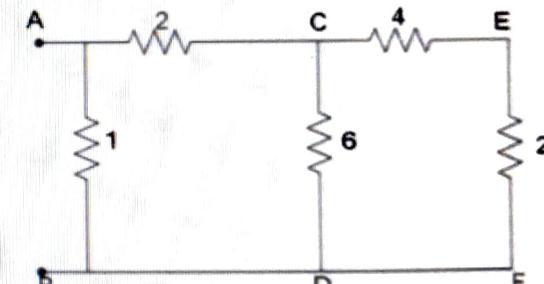


Problem: Equivalent resistance

- Between C & D

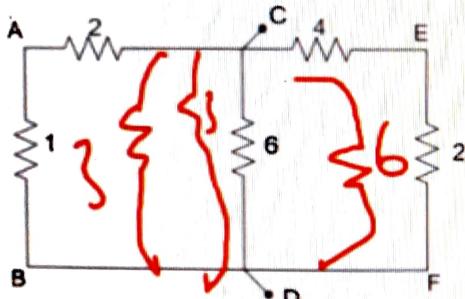


$$\frac{9}{6} = \frac{3}{2} = 1.5$$

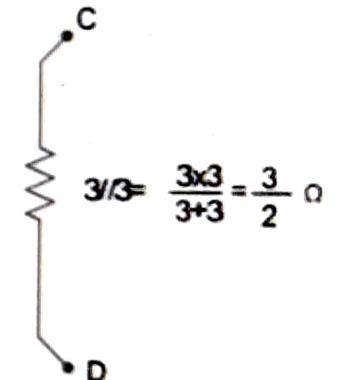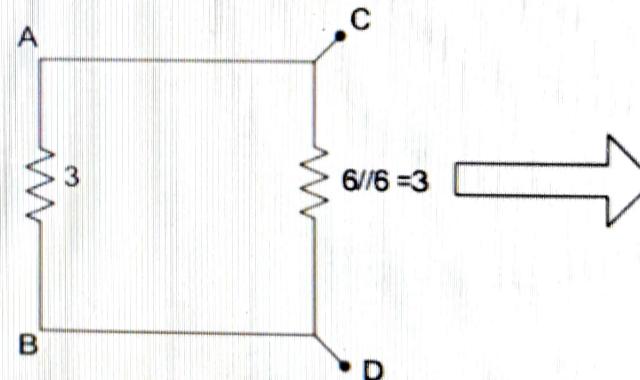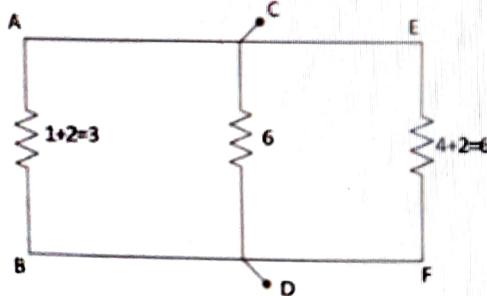

$$R_{C-D} = \frac{3}{2} \Omega$$

R circuit: what is the current flowing?

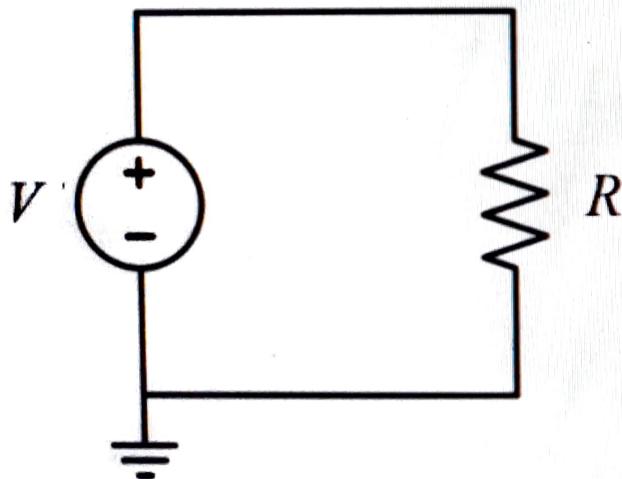

Examples

Immersion water heater



What is the resistance of the coil?




Typical specification of the coil are 1000 W at 230 V

Equivalent voltage sources

$\frac{1}{T}$

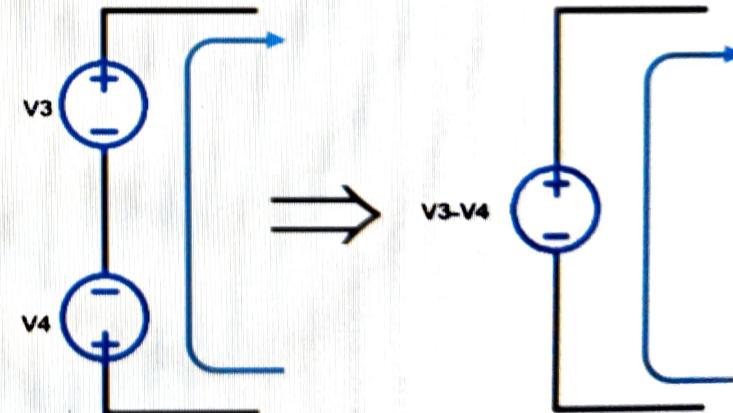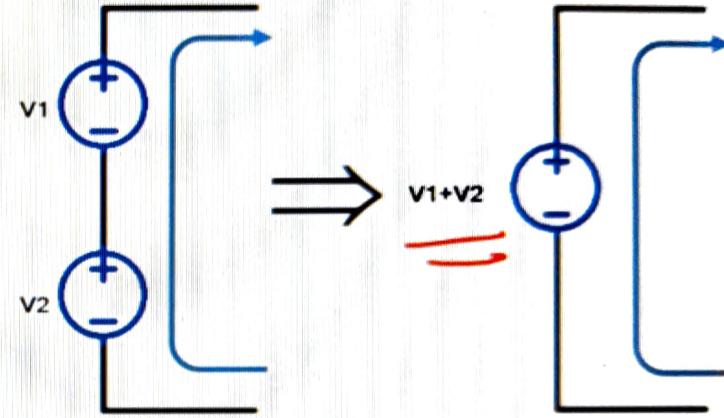


Find i_1 , i_2 and i_3

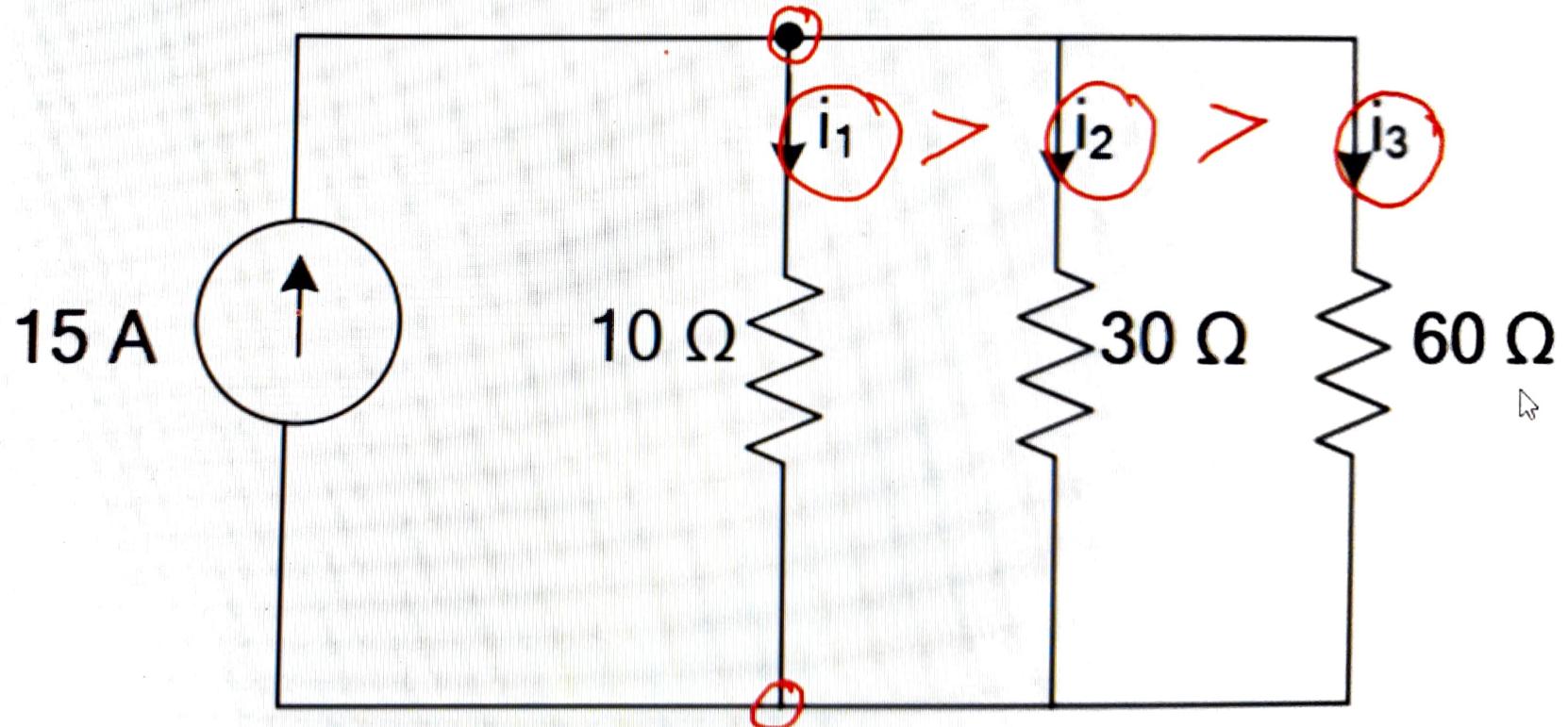


Find i_1 , i_2 and i_3
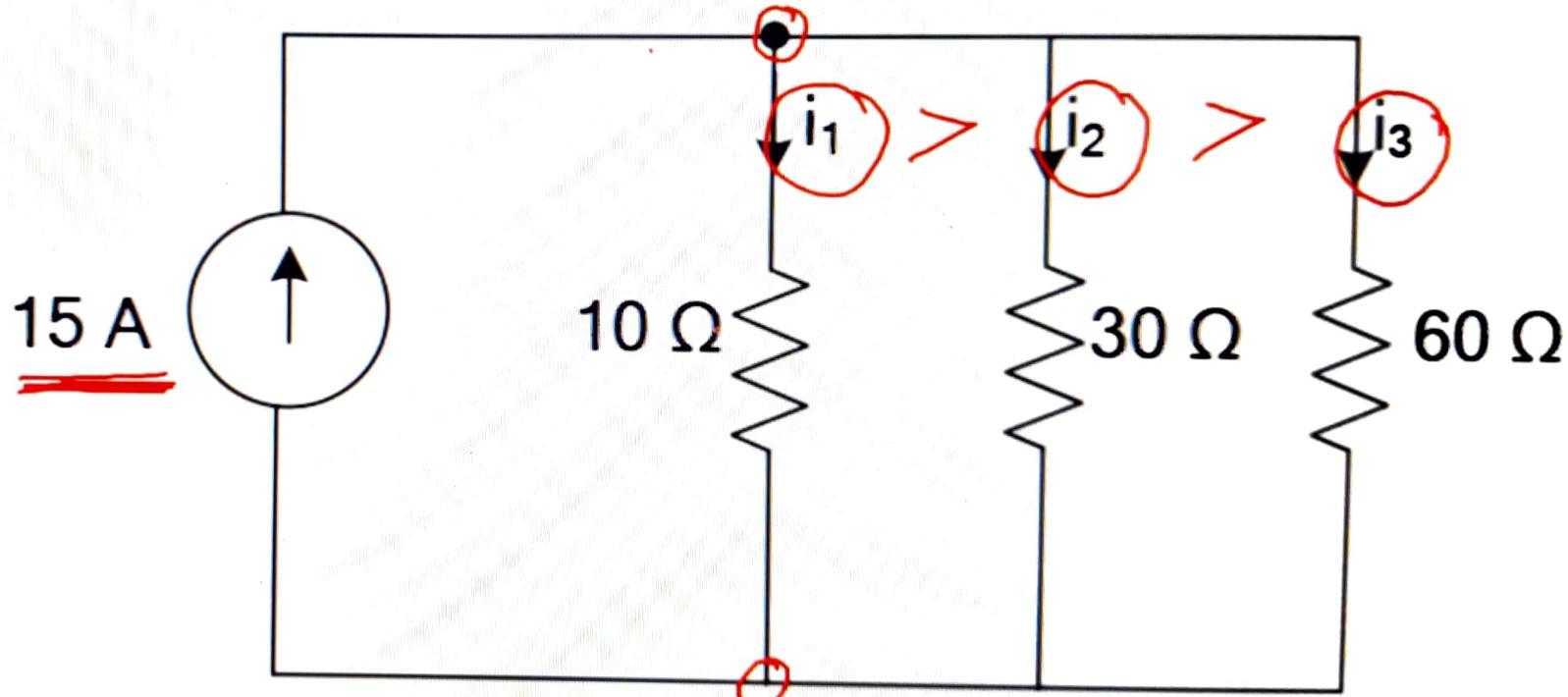
$$i = i_1 \cdot \frac{(30 \times 60)}{30 + 60}$$



- Find i_x

$$i_x = 1.4 \text{ A}$$

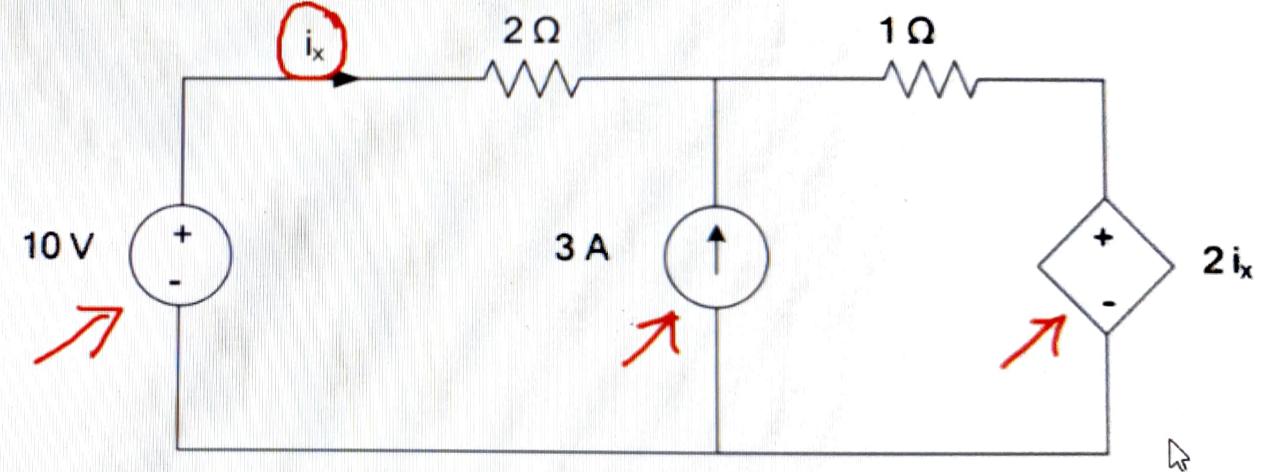


- Find i_x

$$i_x = 1.4 \text{ A} \quad \checkmark$$

\equiv
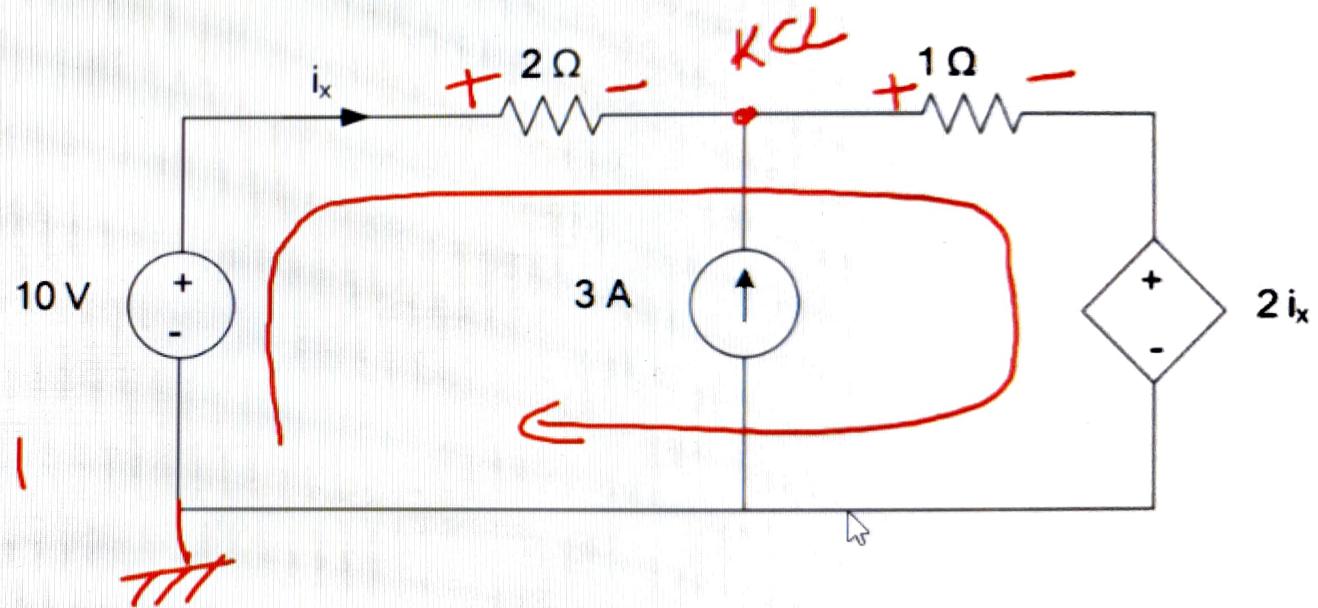
$$-10 + 2i\alpha + (3+i\alpha)^1 \\ + 2i\alpha = 0$$




Node: Any junction point between two or more elements (1,2,3 and 4)

Essential node: A Junction between MORE than two elements (2 and 4)



Non-essential node: A Junction between only two elements (1 and 3)

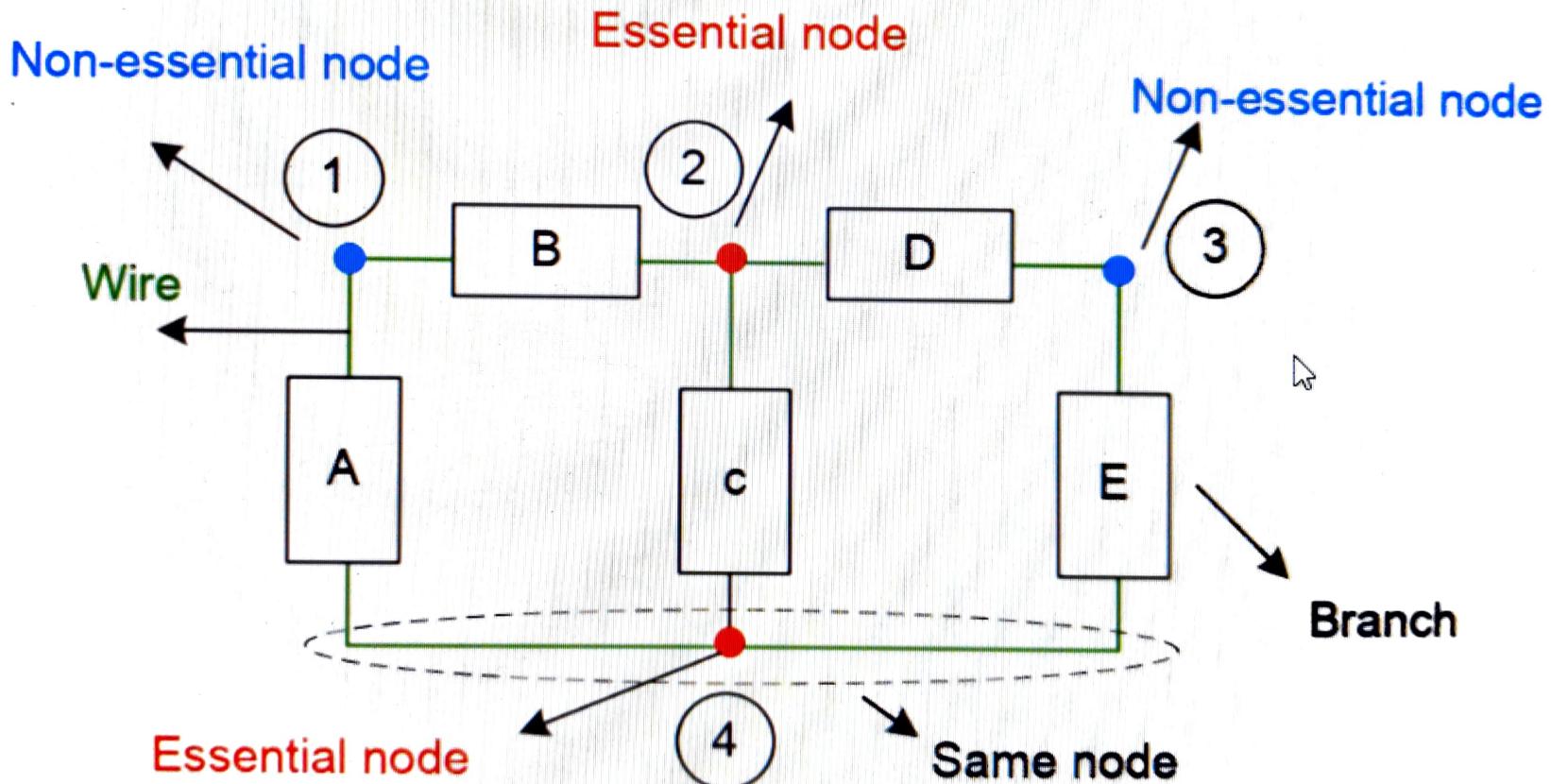Branch: The part of the circuit that lies between two nodes (A,B,C,D and E)




Loop: a closed path in a circuit (loop1, loop2 and loop3)

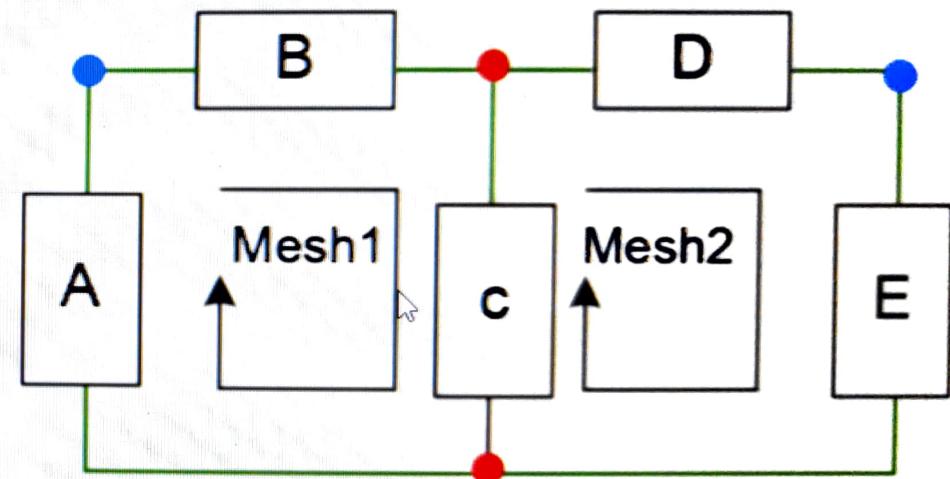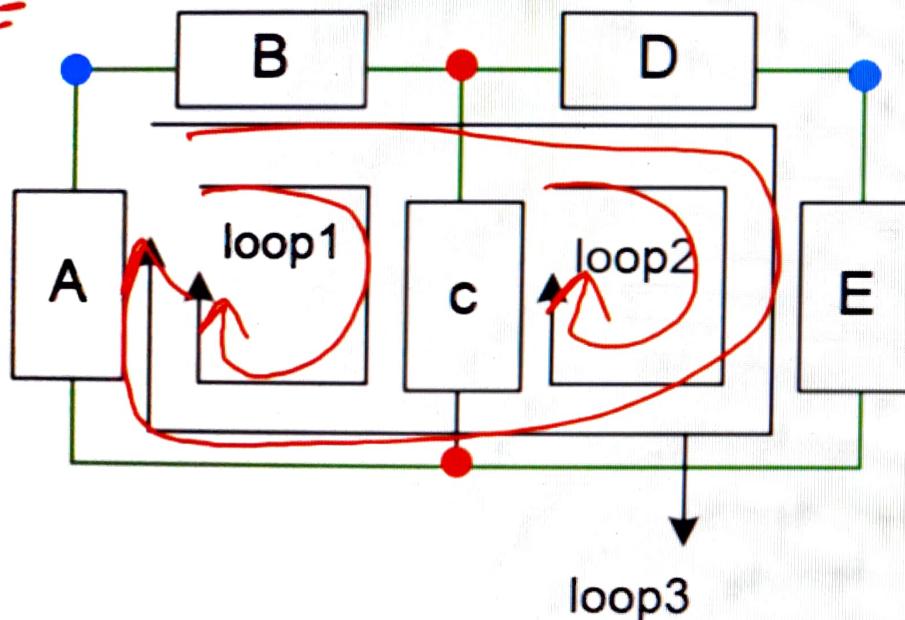
Mesh: a loop that does not contain any loops (Mesh1 and Mesh2)



Double-subscript Notation for Currents:

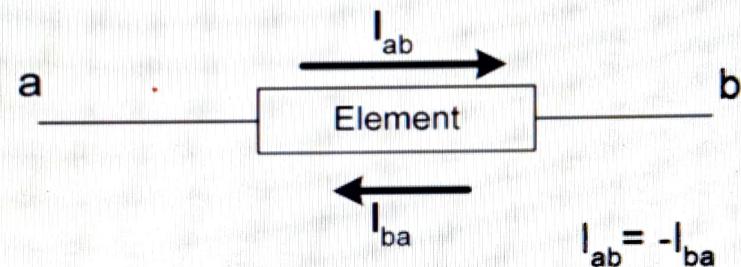


Double-subscript Notation for Voltages:

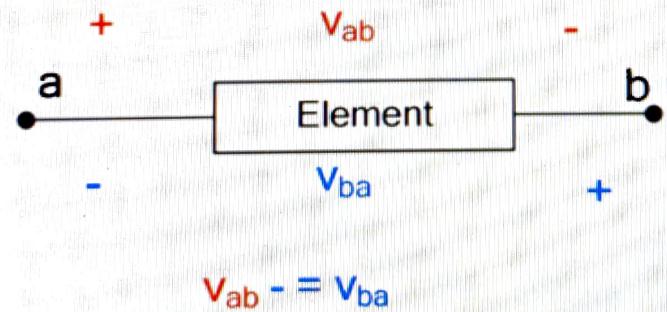

Passive Reference Configuration:

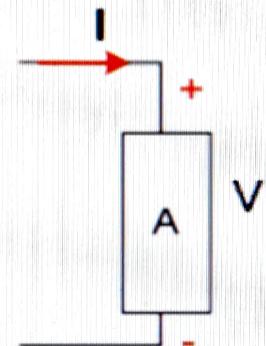In the following figure, notice that the current reference enters the positive polarity of the voltage. This arrangement is called passive reference configuration.




$$P = V \cdot I$$

Note:

If the current reference enters the negative end of the reference polarity we compute the power as:

$$P = -V \cdot I$$

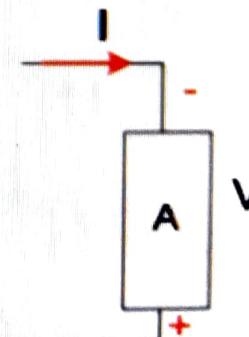


$$P = -V \cdot I$$

A **positive** value for p indicates the energy is **absorbed** by the element and a **negative** value of p shows that the energy is **supplied** by the element

Power is conserved over all any circuit. This means that the magnitude of the supplied power **MUST** be equal to the magnitude of the absorbed power (see the last example of this note).


Example:

Calculate the power for each element.

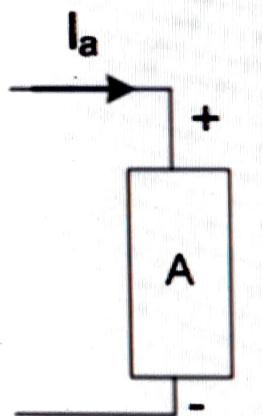


$$V_{a12} = V$$

$$I_{a2} = A$$

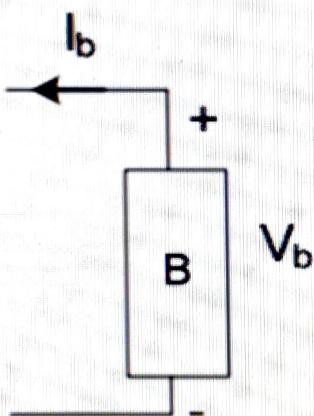

$$V_{b12} = V$$

$$I_{b1} = A$$

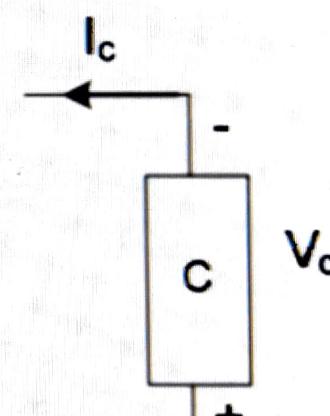

$$V_{c4} = V$$

$$I_{c2} = -A$$

Solution

$$P_a = v_a i_a = 12 \times 2 = 24 \text{ w (Absorbed)}$$

$$P_b = -v_b i_b = -12 \times 1 = -12 \text{ w (Supplied)}$$

$$P_c = v_c i_c = 4 \times (-2) = -8 \text{ w (Supplied)}$$


$$i_1 + 2 = 7$$

$$i_1 = 5 \text{ A}$$

Example:

Find the value of the i_1 and i_2 :


KCL

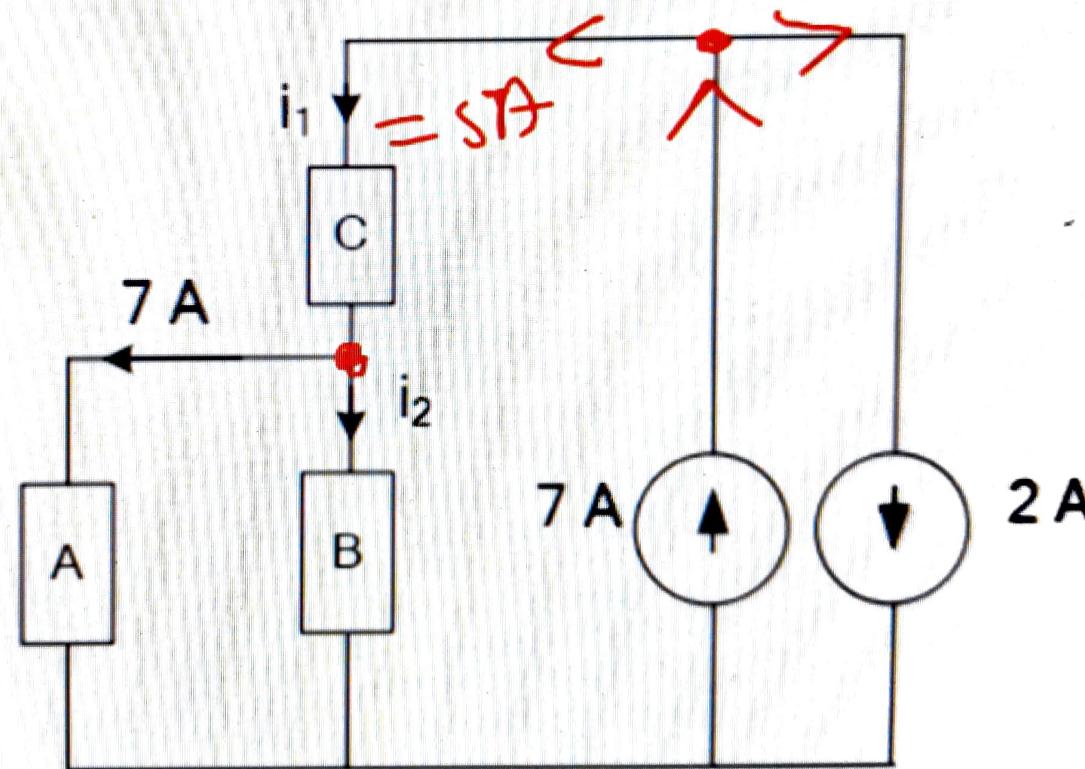

$$V_1 = V_2$$

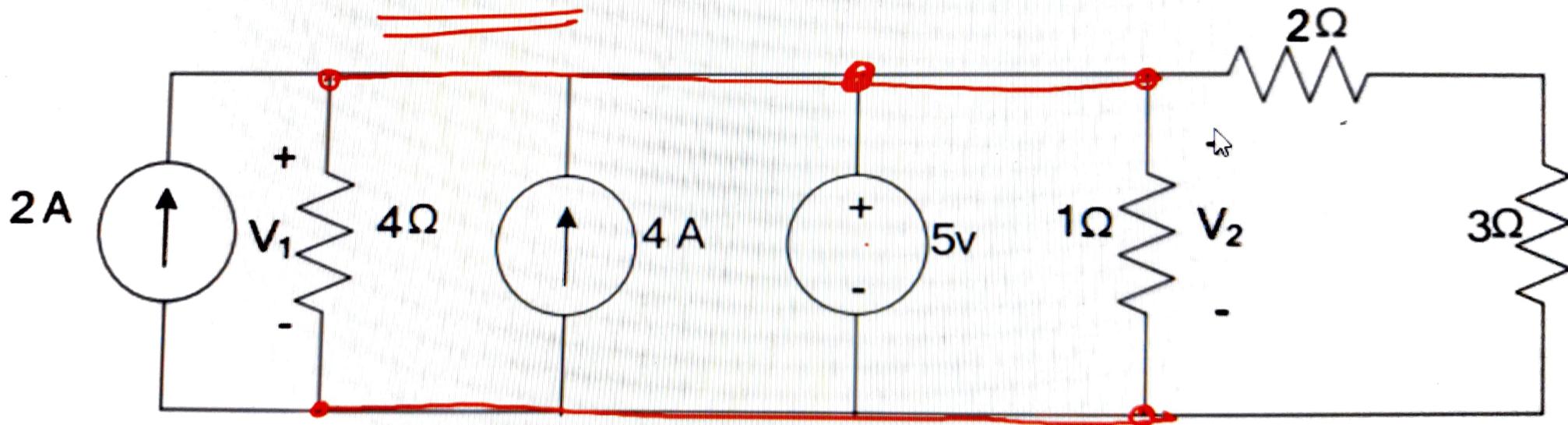Example:


In the following circuit find V_1 and V_2 .



For the following circuit

a. Find V_x and R .

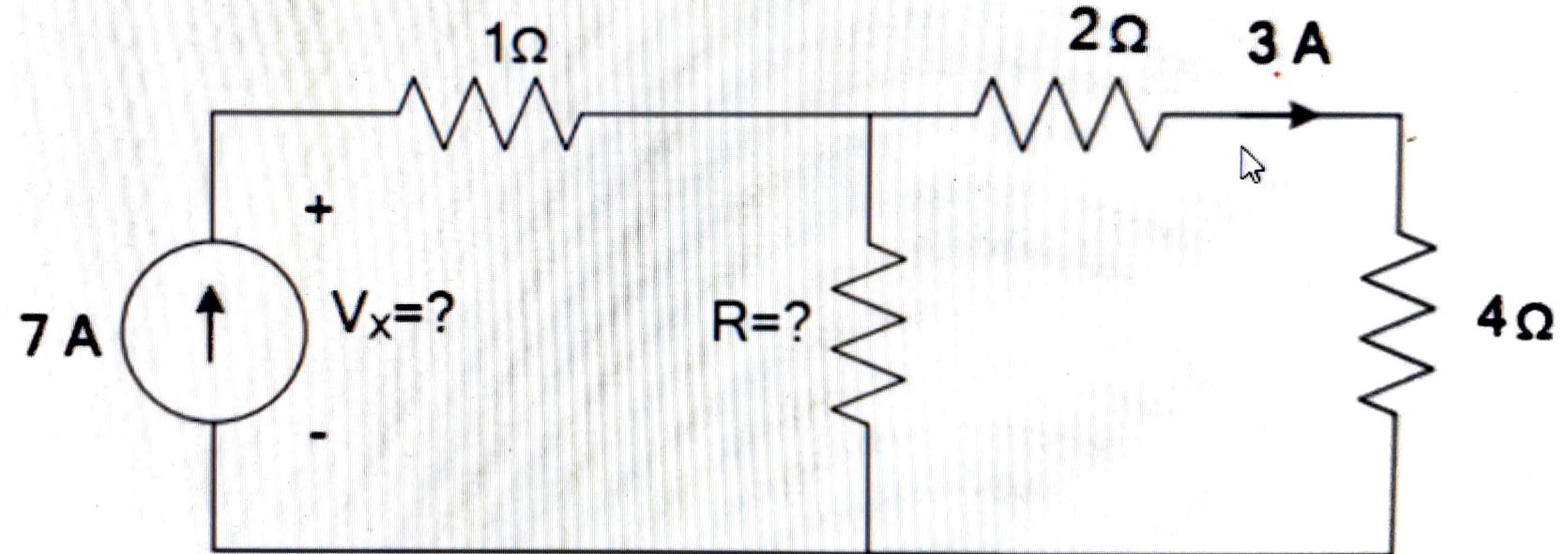
b. Prove that the supplied power is equal to the absorbed power.



For the following circuit

a. Find V_x and R .

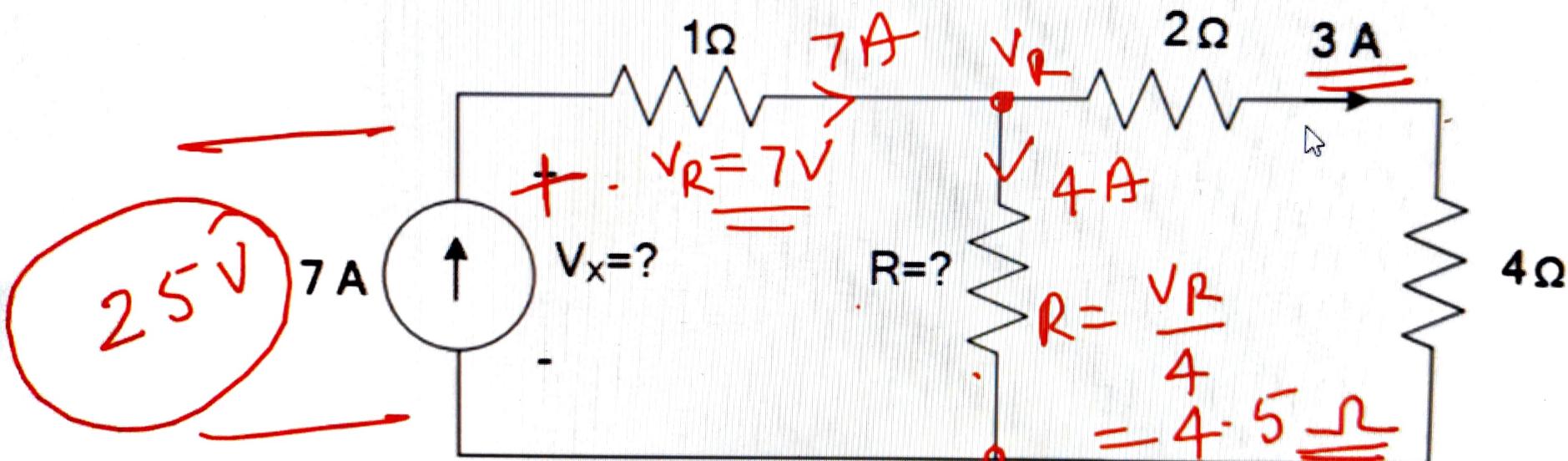b. Prove that the supplied power is equal to the absorbed power.




$$R = 2 + 4 = 6\Omega$$


$$V_R = 6 \times 3 = 18V$$

$$i_x = i_1 - i_2$$


- Find i_1 , i_2 and i_x .

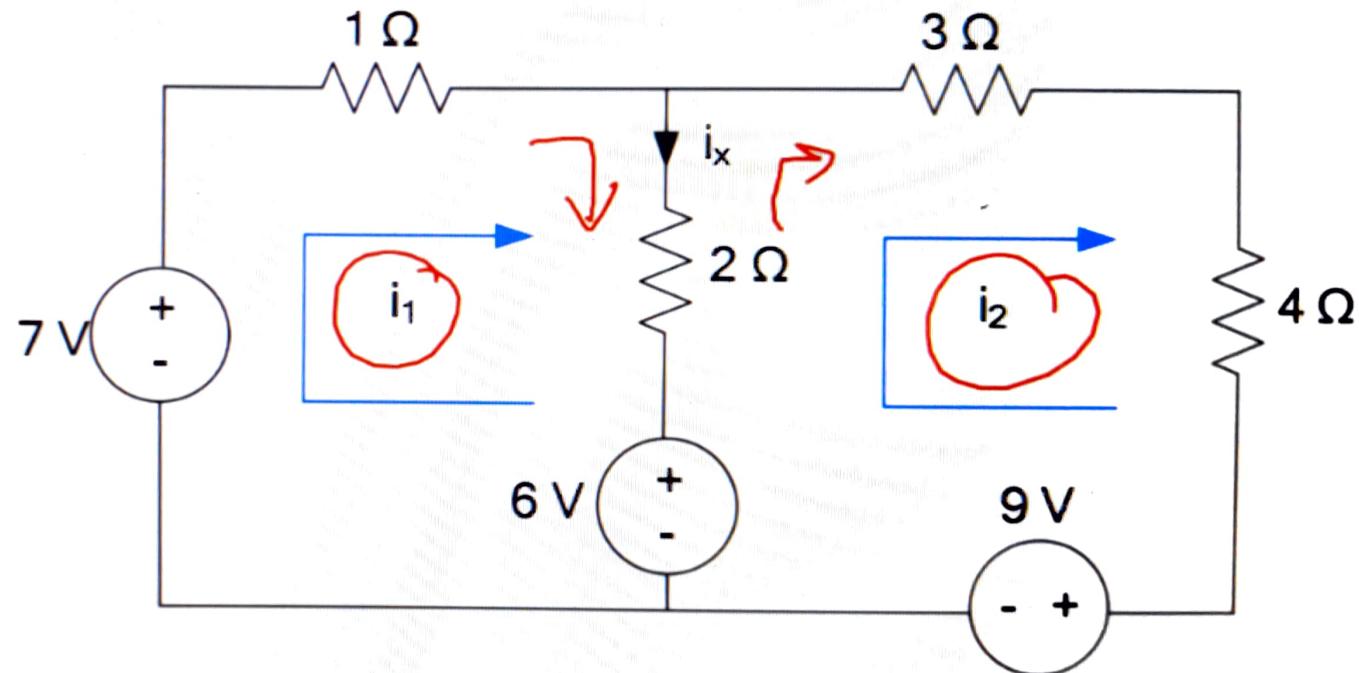

find i_x , i_y and v

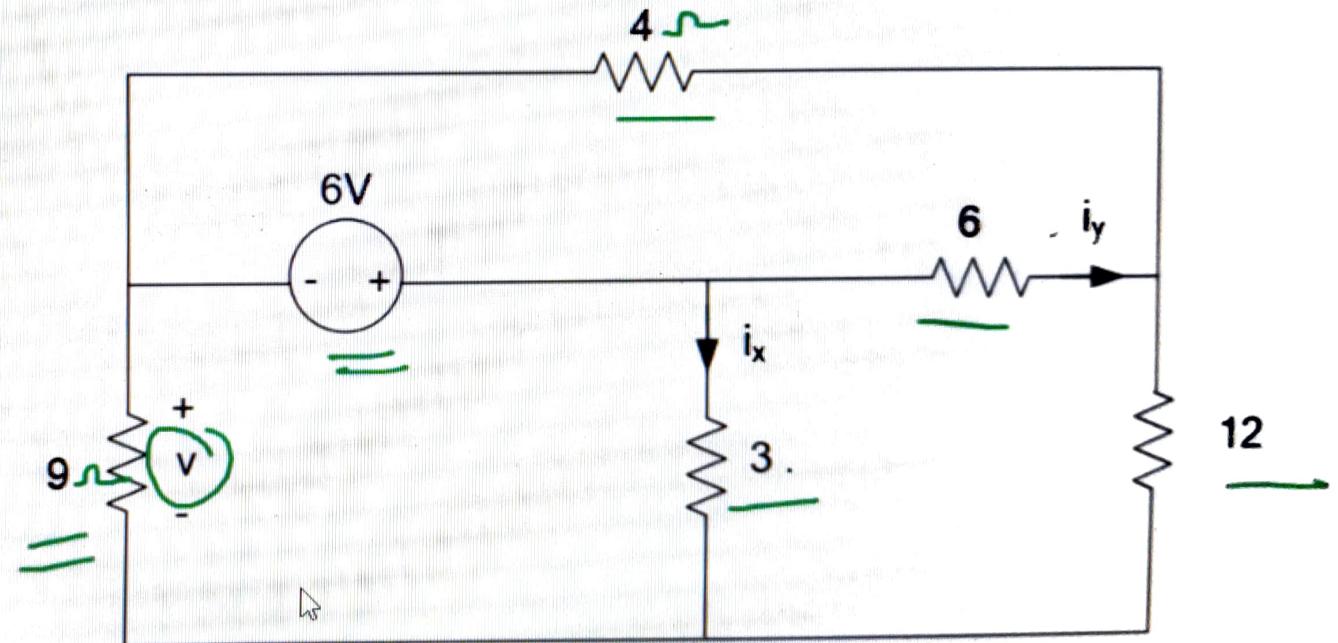

Find V_o

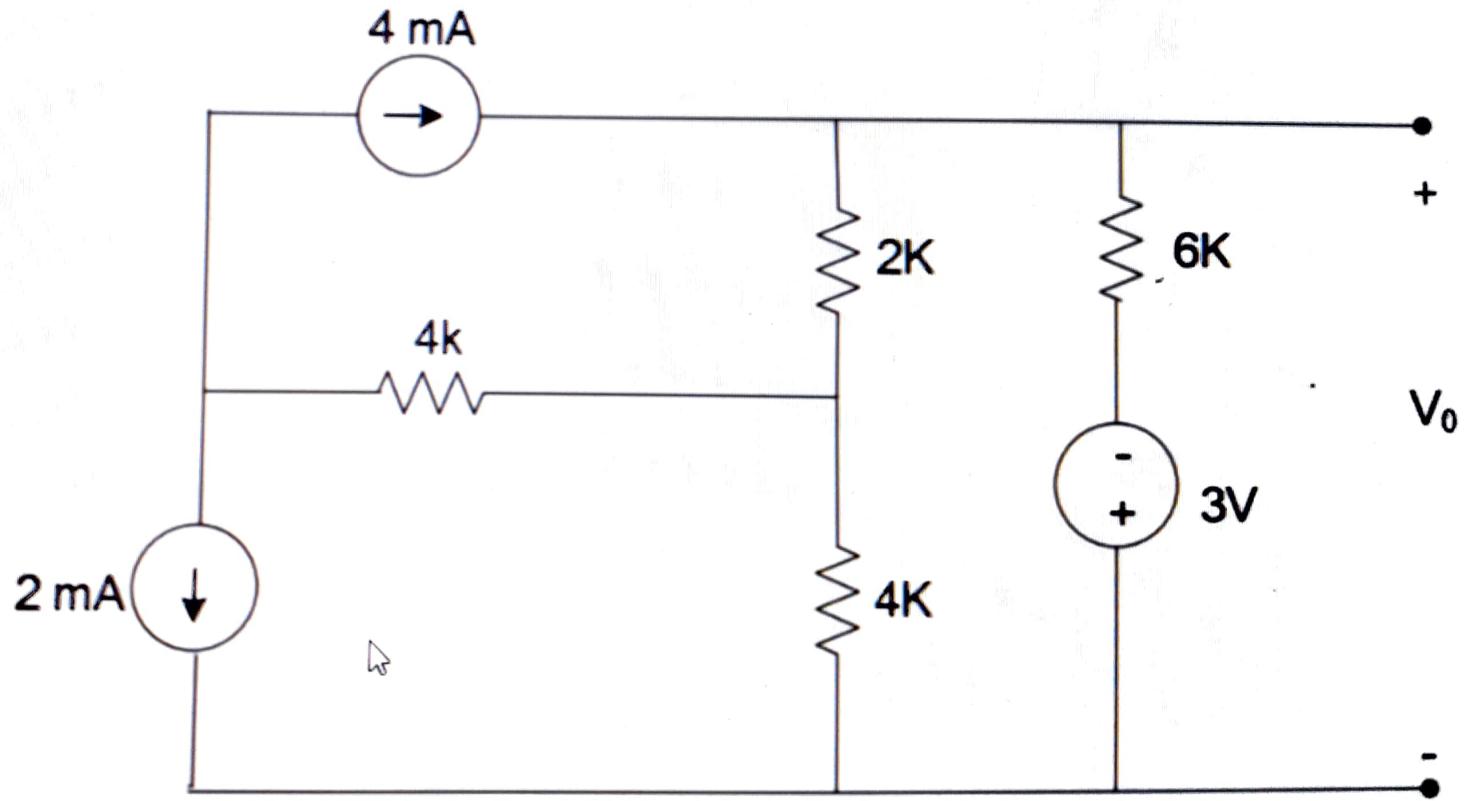

Find V_o

