

Application of Diodes: Logic Gates




- The **logic OR** function
 - $Y=A+B+C$
- The **logic AND** function
 - $Y=A \cdot B \cdot C$

If

v_A Logic High, D_A is RB

v_B Logic High, D_B is RB

v_C Logic LOW, D_B is FB

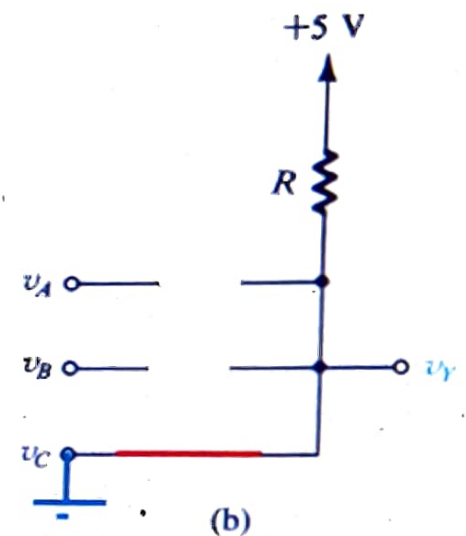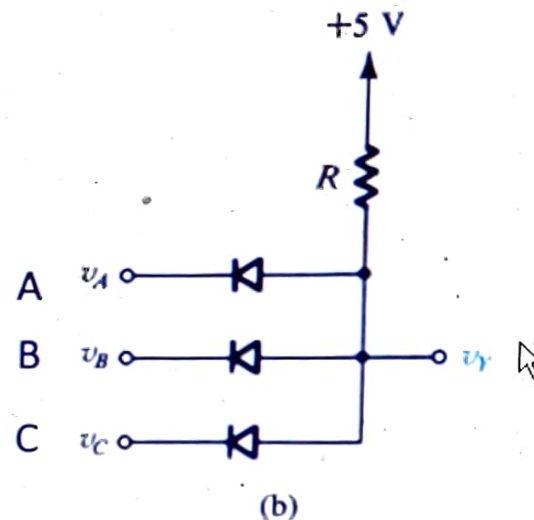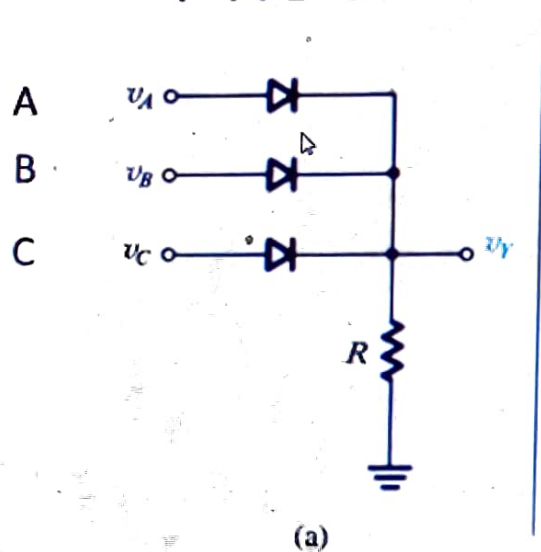

Application of Diodes: Logic Gates




- The **logic OR** function
 - $Y=A+B+C$
- The **logic AND** function
 - $Y=A \cdot B \cdot C$

If


v_A Logic High, D_A is RB

v_B Logic High, D_B is RB

v_C Logic LOW, D_C is FB

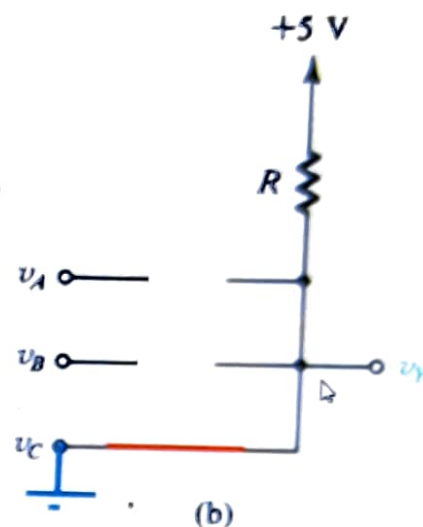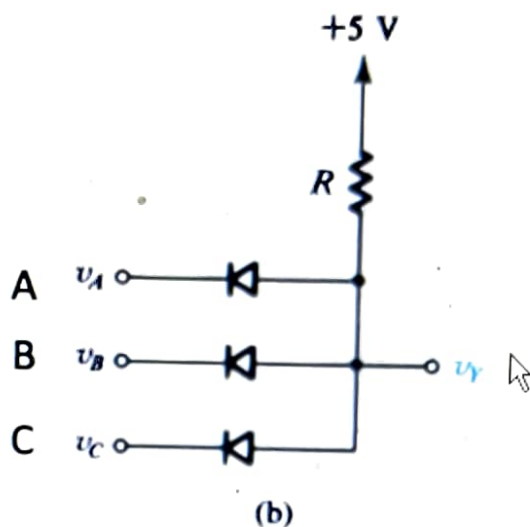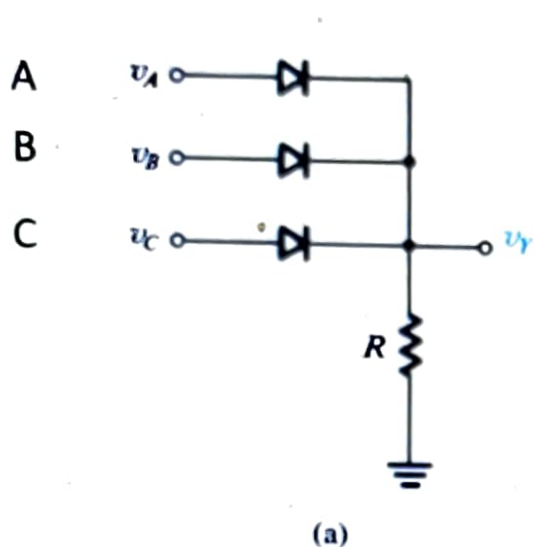


Potential drop in Diode

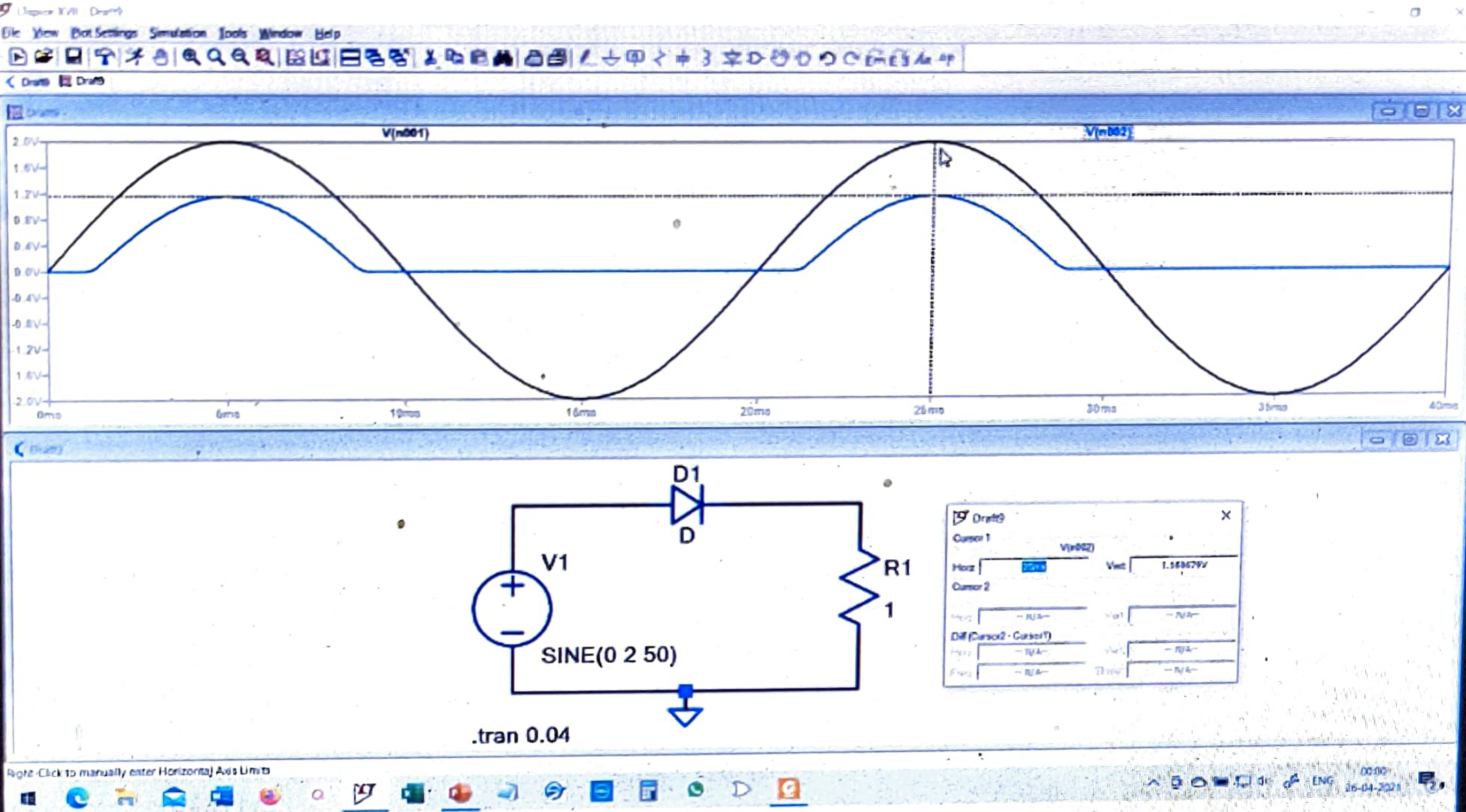


Find V and I


- Assume ideal diodes

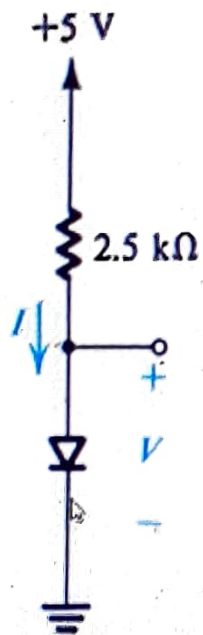


(a)

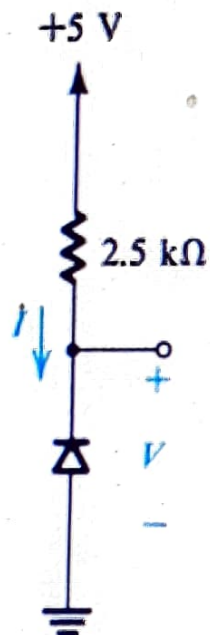

(b)

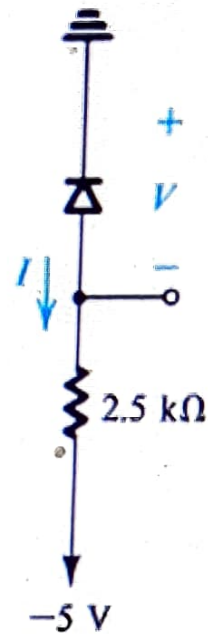


(c)

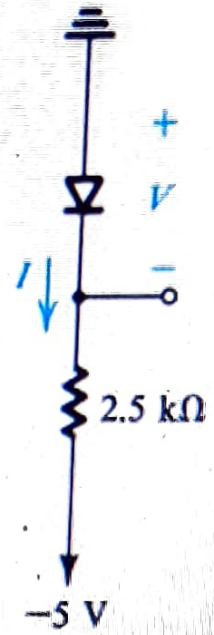

(d)

Find V and I

- Assume ideal diodes

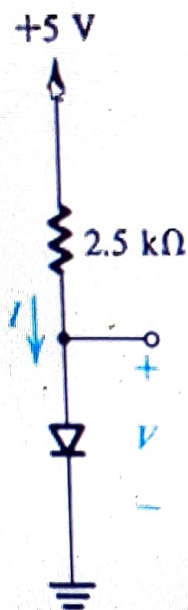


(a)

Diode is FB, Therefore short circuit, $V = 0\text{ V}$

$$I = \frac{5 - 0}{2.5k} = 2\text{ mA}$$

Find V and I


- Assume ideal diodes

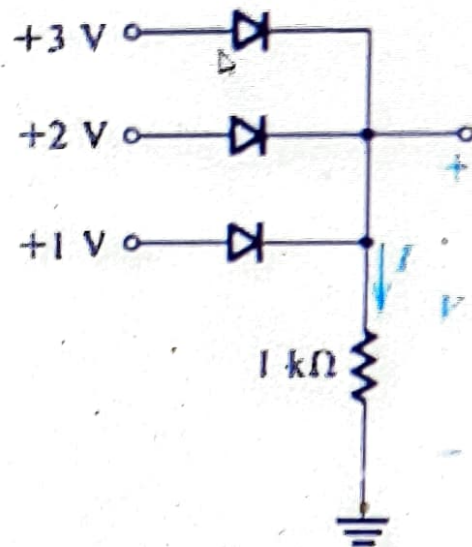

(e)

$$V = 3V$$


$$I = \frac{3}{1k} = 3mA$$

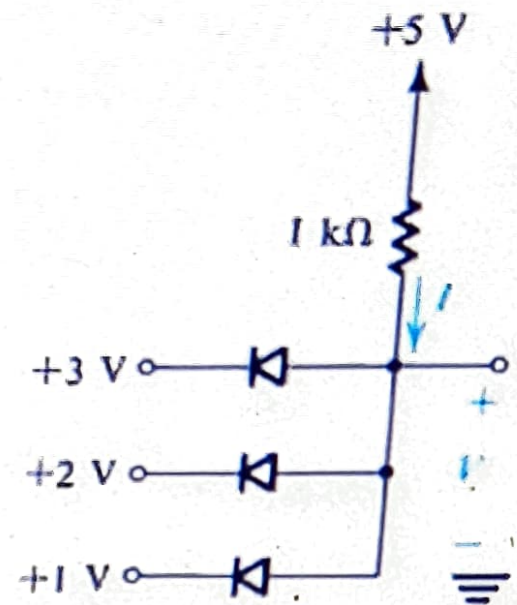

(f)



Diode circuits

- Find current 'i'

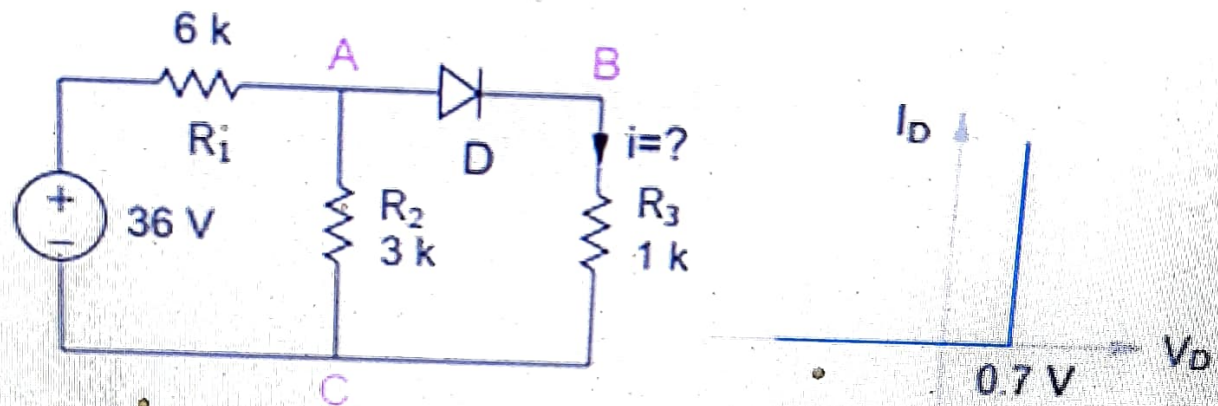

Diode circuits

- Case 1: Assume diode 'D' is OFF

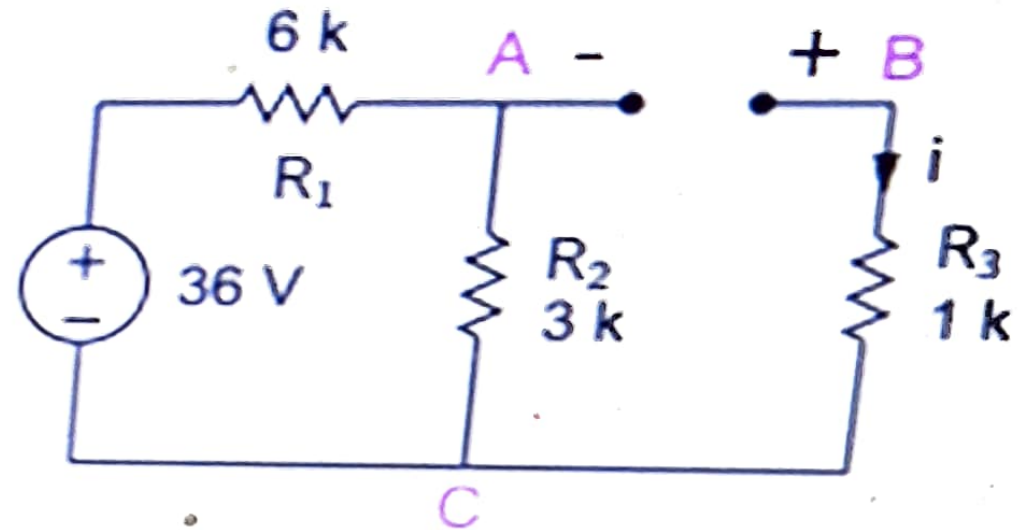
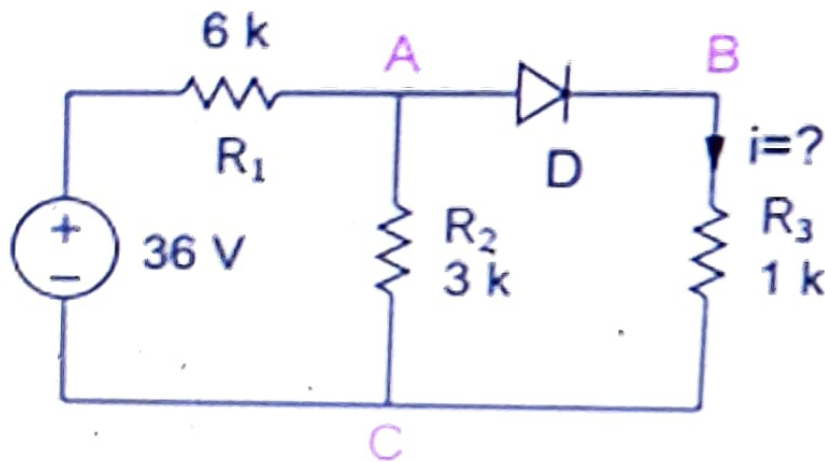


$$V_{AB} = \frac{3}{3+6} \times 36 = 12 \text{ V}$$

Assumption and solution are inconsistent, therefore diode is not OFF

Diode circuits

- Case 2: Assume diode 'D' is ON

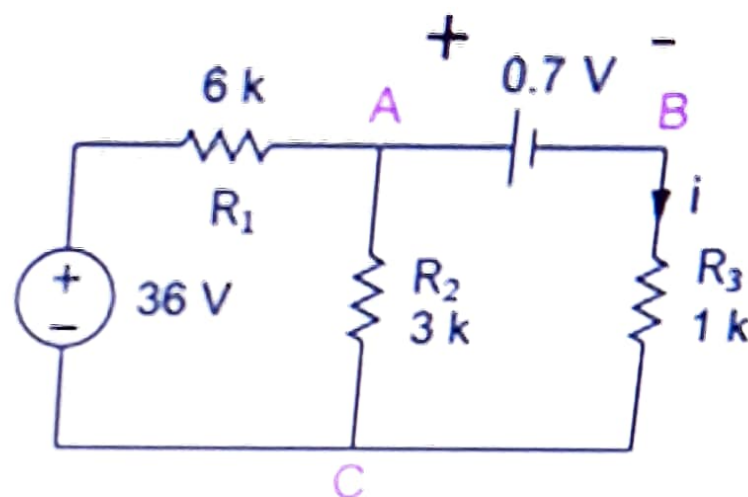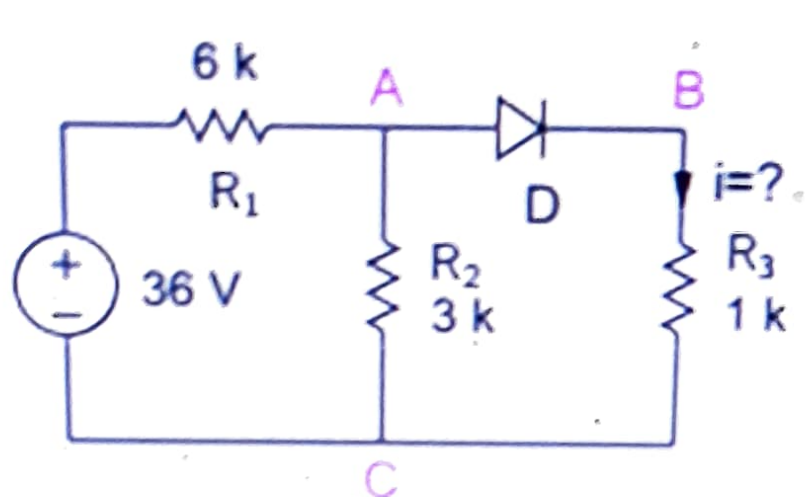


Using Nodal analysis

$$\frac{V_A - 36}{6K} + \frac{V_A}{3K} + \frac{V_A - 0.7}{1K} = 0 \Rightarrow V_A = 4.47 \text{ V}$$

$$i = 3.77 \text{ mA}$$

Assumption and solution are consistent, therefore diode is ON

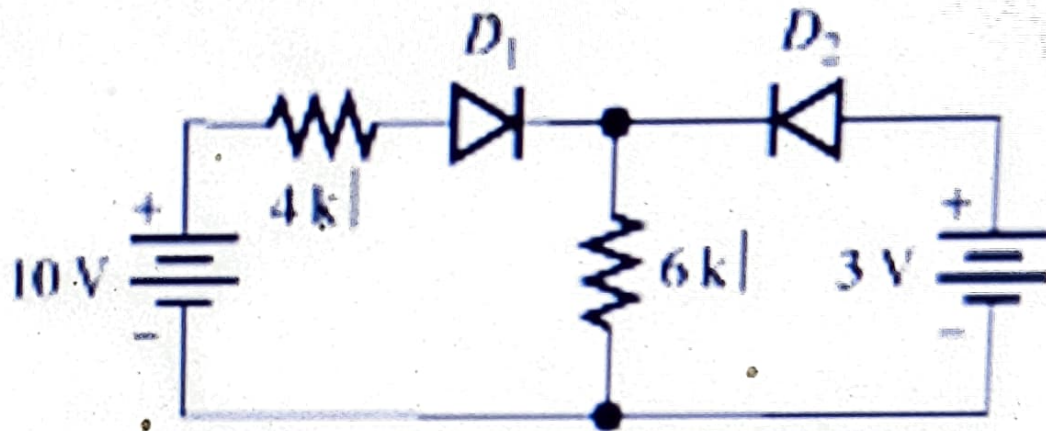- Find current flowing in $6\text{k}\Omega$ resistor. Assume ideal diode model



- Find V and I . Assume diodes to be ideal.

