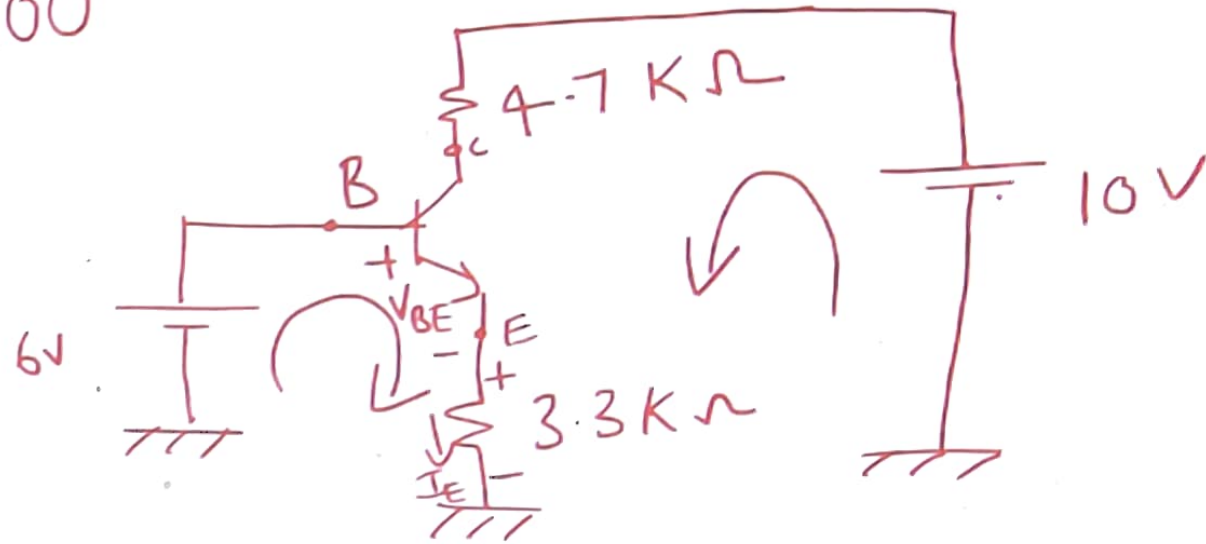


$$\beta = 100$$



$$-6 + 0.7 + (3.3 \text{ k}) I_E = 0 \Rightarrow I_E = 1.6 \text{ mA}$$


$$I_E = I_B + I_C = I_B + \beta I_B = (1 + \beta) I_B$$

$$I_B = 15.84 \mu\text{A}, I_C = 1.58 \text{ mA}$$

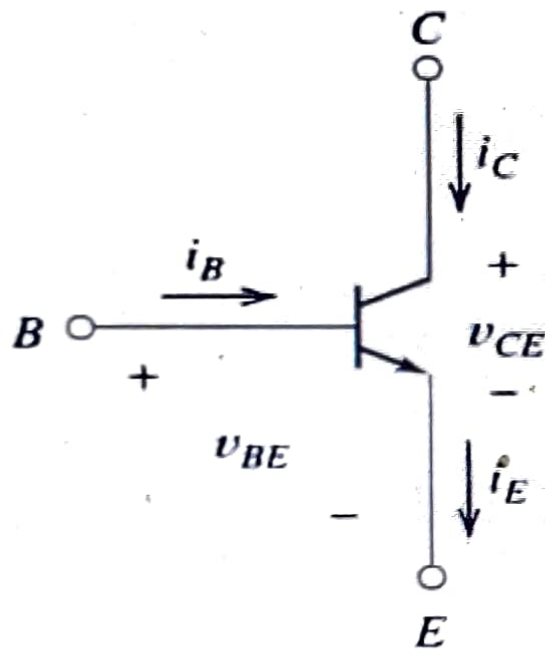Problem

Suppose that a certain *npn* transistor has $V_{BE} = 0.7 \text{ V}$ for $I_E = 10 \text{ mA}$. Compute V_{BE} for $I_E = 1 \text{ mA}$.

Repeat for $I_E = 1 \mu\text{A}$. Assume that $V_T = 26 \text{ mV}$.



$$I_E = I_{ES} \left(\exp\left(\frac{V_{BE}}{V_T}\right) - 1 \right) \approx I_{ES} \exp\left(\frac{V_{BE}}{V_T}\right)$$

$$10 \text{ mA} = I_{ES} \exp\left(\frac{0.7}{0.026}\right) \quad \text{and} \quad 1 \text{ mA} = I_{ES} \exp\left(\frac{V_{BE}}{0.026}\right)$$


$$\text{divide the above} \Rightarrow 10 = \exp\left(\frac{0.7 - V_{BE}}{0.026}\right)$$

$$\Rightarrow 0.026 \times \ln 10 = 0.7 - V_{BE}$$

$$\therefore V_{BE} = 0.7 - 0.026 \times \ln 10 = 0.64 \text{ V}$$

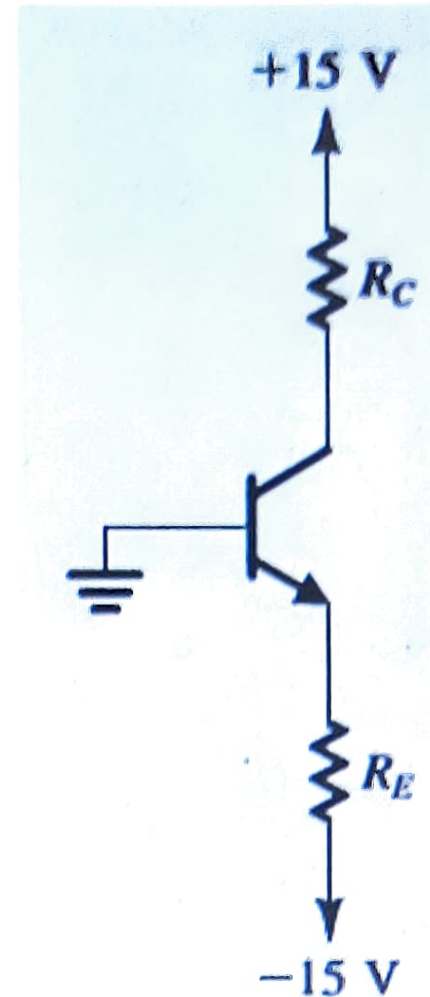
Problem

- The transistor in the circuit of Fig. has $\beta = 100$ and exhibits a v_{BE} of 0.7 V at $i_C = 1\text{ mA}$. Design the circuit so that a current of 2 mA flows through the collector and a voltage of $+5\text{ V}$ appears at the collector.



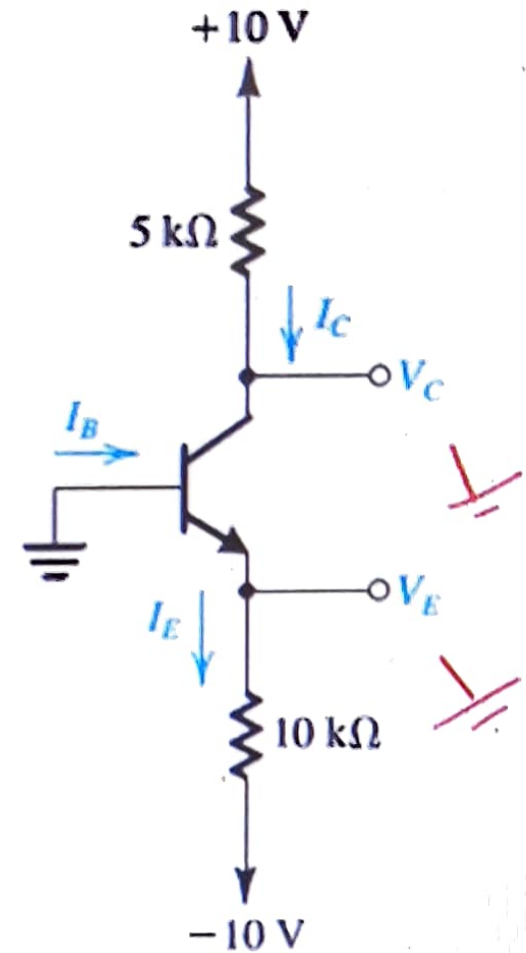
Problem

- In the circuit shown in Fig., the voltage at the emitter was measured and found to be -0.7 V. If $\beta = 50$, find I_E , I_B , I_C , and V_C .



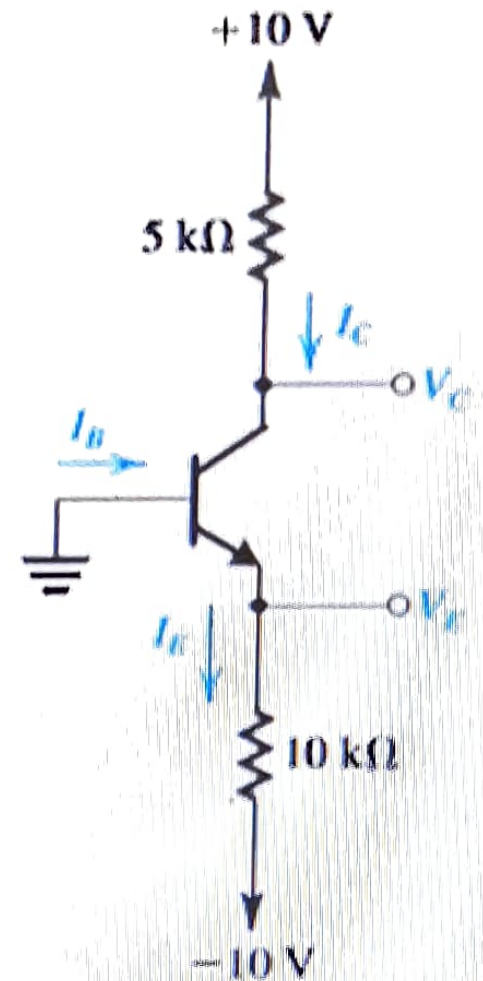Problem

- In the circuit shown in Fig., measurement indicates V_B to be +1.0 V and V_E to be +1.7 V. What are α and β for this transistor? What voltage V_C do you expect at the collector?




Problem

Consider the circuit shown in Figure. Transistors Q_1 and Q_2 are identical, both having $I_{ES} = 10^{-14} \text{ A}$ and $\beta = 100$. Calculate V_{BE} and I_{C2} . Assume that $V_T = 26 \text{ mV}$ for both transistors.

Hint: Both transistors are operating in the active region.

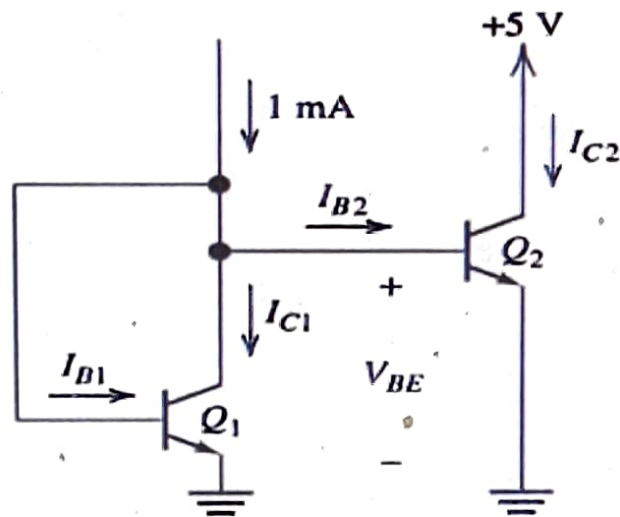Because the transistors are identical and have identical values of V_{BE} , their collector currents are equal.



$$I_{B1} + I_{B2} + I_C = 1 \text{ mA} \quad \& \quad I_C = \beta I_B$$

$$\Rightarrow I_C \left(\frac{2}{\beta} + 1 \right) = 1 \text{ mA} \Rightarrow I_C = \frac{1 \text{ mA}}{1.02} = 0.98 \text{ mA}$$

$$I_E = \left(1 + \frac{1}{\beta} \right) I_C = 0.99 \text{ mA}$$

$$\text{since } I_E \approx I_{ES} \exp\left(\frac{V_{BE}}{V_T}\right) \text{ we have}$$

$$\therefore V_{BE} = V_T \ln \frac{I_E}{I_{ES}} = 0.026 \times \ln(0.99 \times 10^{-11}) = 0.658 \text{ V}$$

Problem

- Find currents and voltages

