

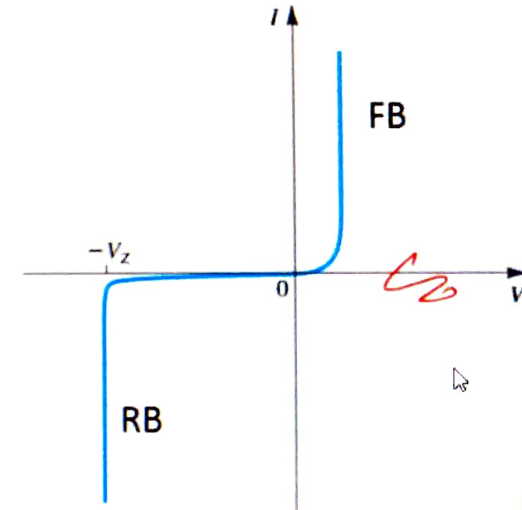



# Transistor as an amplifier

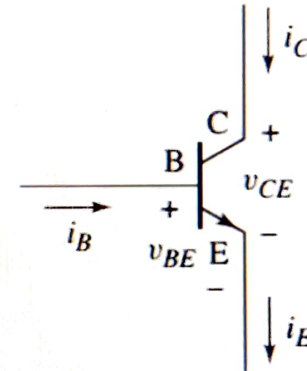

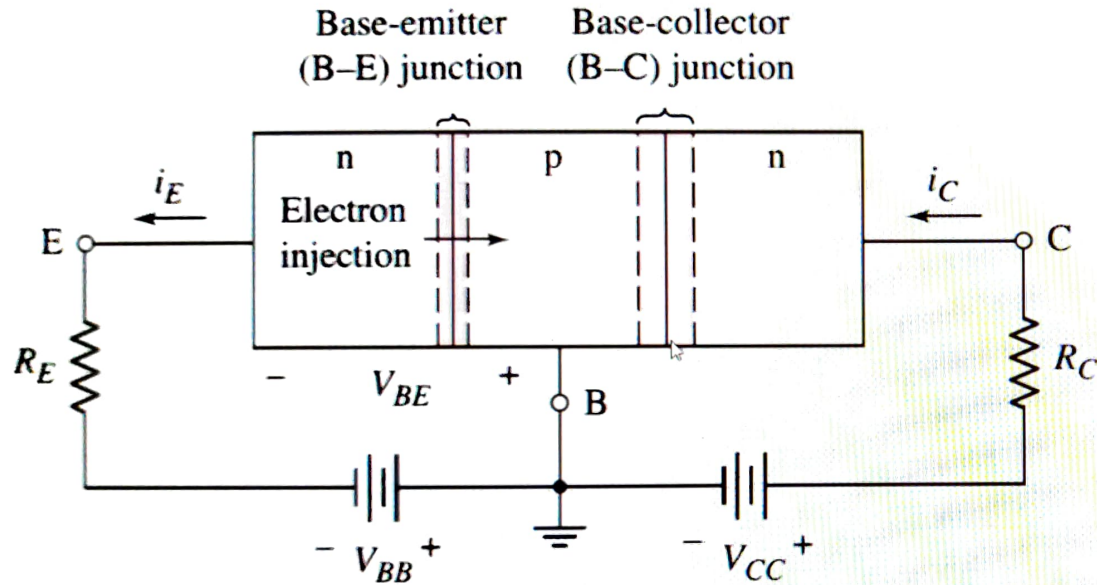Current flow in a *nnp* transistor biased to operate in the active mode


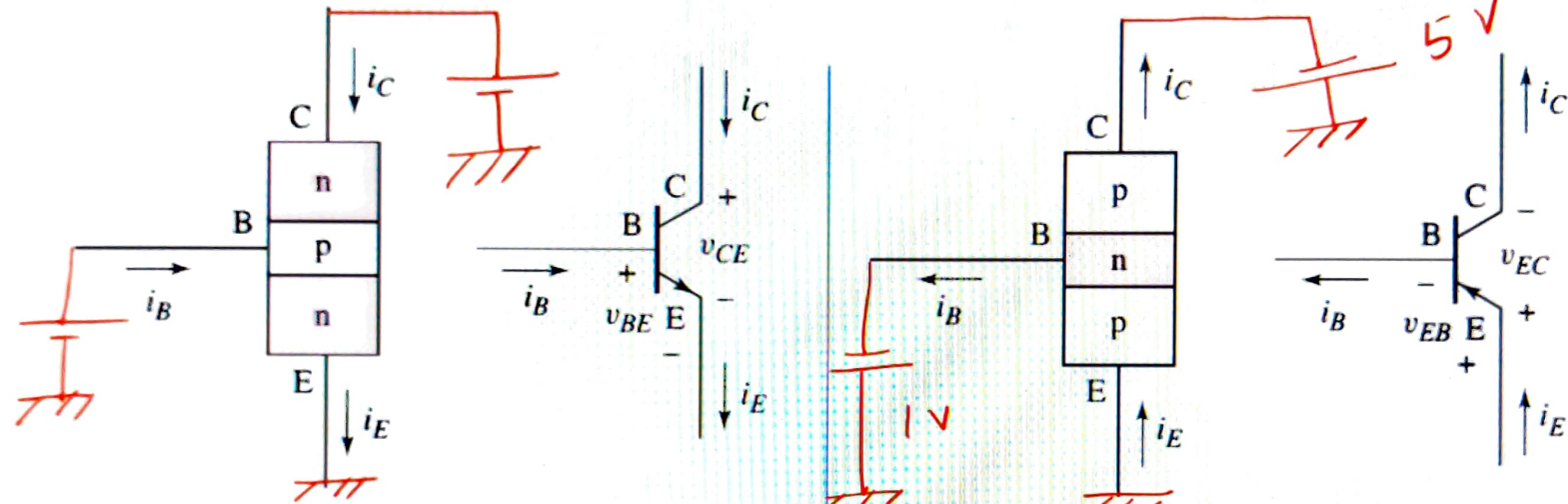
# Block diagrams and circuit symbols for BJT



**NPN transistor**

majority - electrons

mobility  $\mu_n > \mu_p$



**PNP transistor**

holes


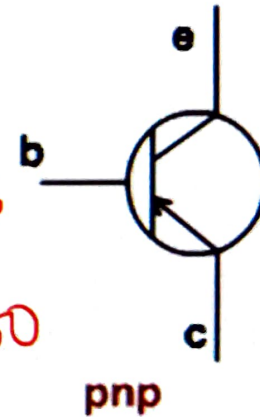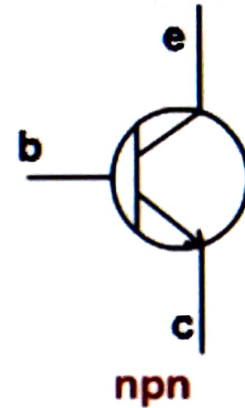
# Currents in BJT

- The total current flowing into the transistor must be equal to the total current flowing out of it
- the emitter current  $I_E$  is equal to the sum of the collector ( $I_C$ ) and base current ( $I_B$ )



$$I_E = I_C + I_B$$

$$I_C = \alpha I_E$$

$$I_C = \beta I_B$$

$\alpha$  = Common base current gain

$\beta$  = Common emitter current gain

$$I_C = I_S e^{V_{BE}/V_T}$$

$$\beta = \frac{\alpha}{1 - \alpha}$$

$$\alpha = \frac{\beta}{1 + \beta}$$

$$I_C = \beta I_B$$

$$\alpha = 1 = 0.9996$$

$$\beta = 50 - 250$$



# Problem

**Objective:** Calculate the collector and emitter currents, given the base current and current gain.

Assume a common-emitter current gain of  $\beta = 150$  and a base current of  $i_B = 15 \mu\text{A}$ . Also assume that the transistor is biased in the forward-active mode.

**Solution:** The relation between collector and base currents gives

$$i_C = \beta i_B = (150)(15 \mu\text{A}) \Rightarrow 2.25 \text{ mA}$$

and the relation between emitter and base currents yields

$$i_E = (1 + \beta)i_B = (151)(15 \mu\text{A}) \Rightarrow 2.27 \text{ mA}$$

the common-base current gain is


$$\alpha = \frac{\beta}{1 + \beta} = \frac{150}{151} = 0.9934$$





# Common emitter amplifier circuit

$$-V_{BB} + i_B R_B + v_{BE} = 0$$

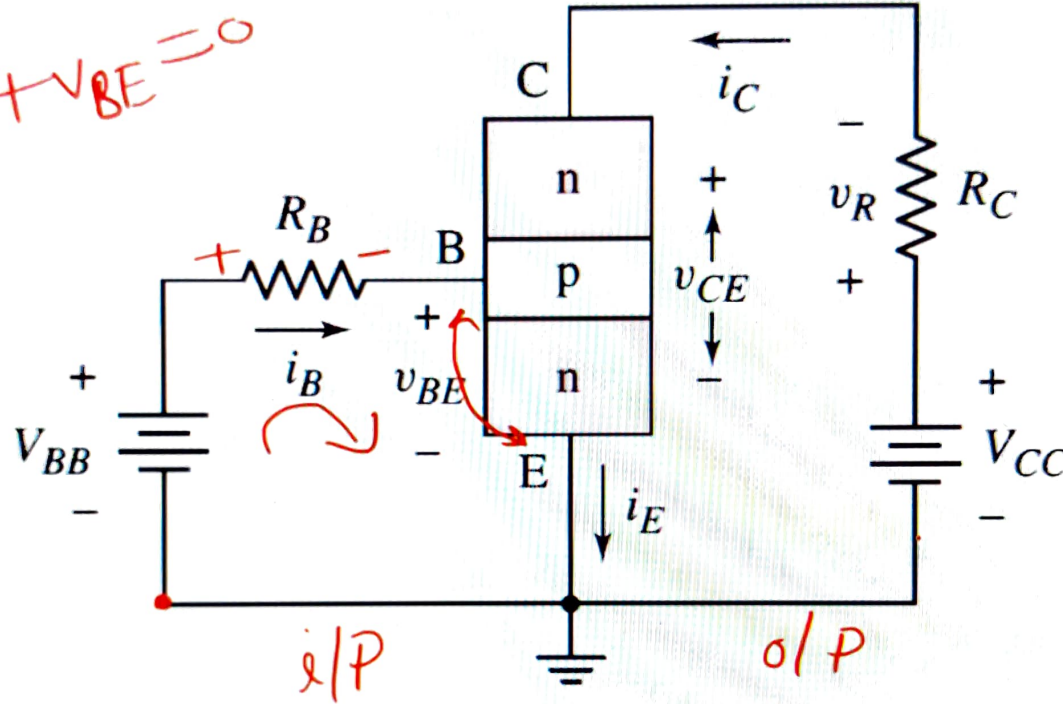

KVL?



Raise hand




Turn on captions



Paul Brain  
is presen

# Common emitter amplifier circuit

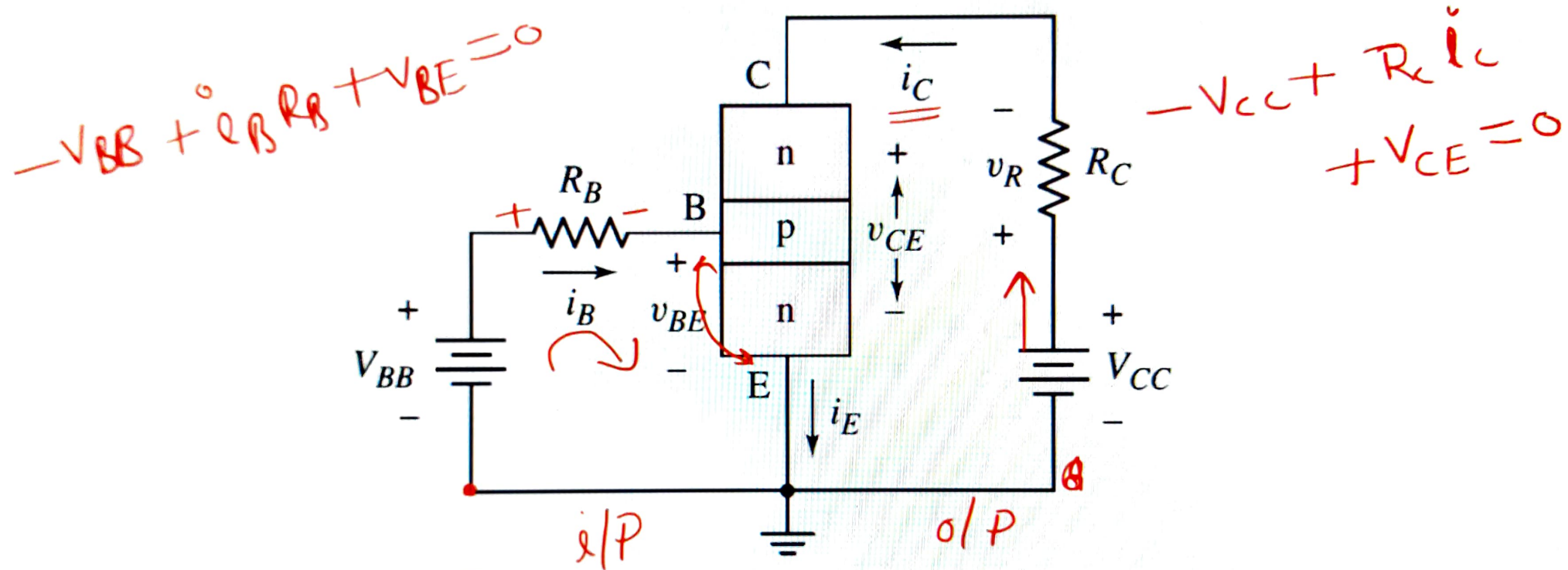

KVL?




# Common emitter circuits

$$V_{BE} = 0.7 \text{ V}$$

$$V_{EB} = -0.7 \text{ V}$$


$$V_{BE} = V_B - V_E = -(V_E - V_B)$$

$$= -V_{EB}$$

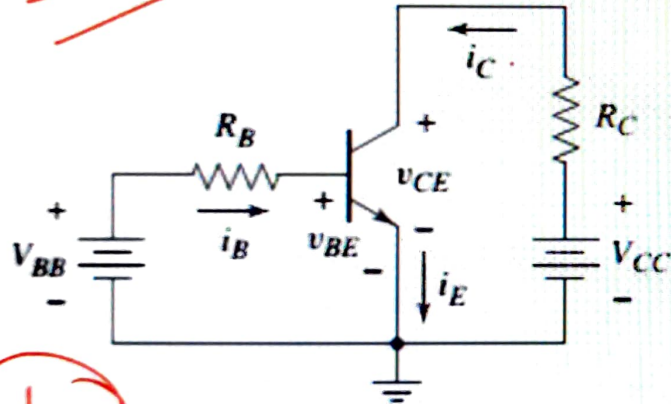

$V_{BE}$

NPN transistor

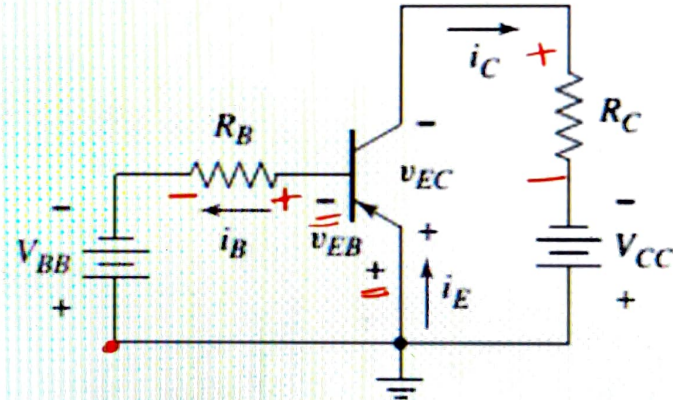


PNP transistor


$$V_{BB} - i_B R_B - V_{EB} = 0$$

# Input and output characteristics of BJT

$V = IR$   
 $y = mx$   
 linear

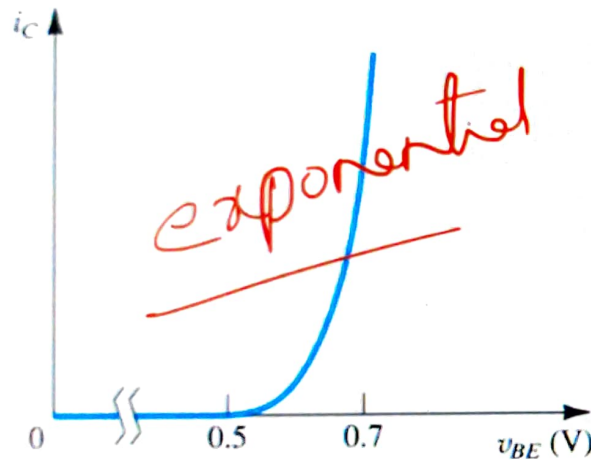

2/P

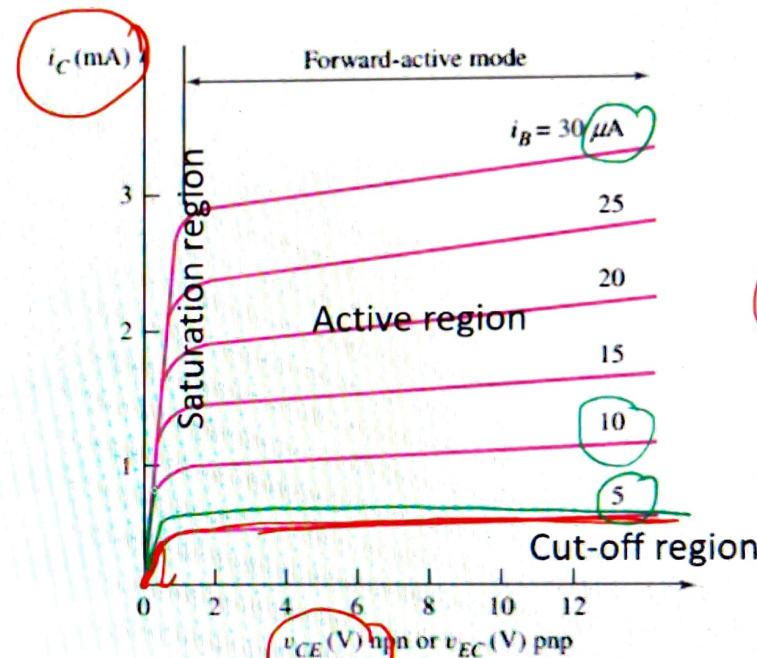

0/P



Raise hand



Turn on captions




Paul Brai  
is present



Find the transistor currents and voltages in the circuit shown in fig. if  $I_{CO} = 20\text{nA}$ ,  $\beta = 100$

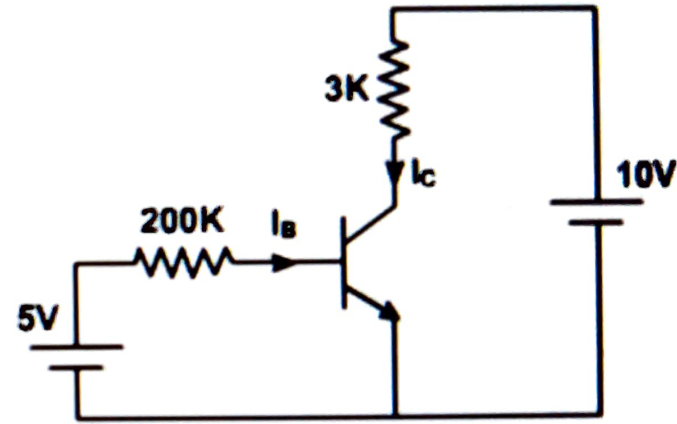
- For the base circuit,  $5 = 200 \times I_B + 0.7$
- Therefore,  $I_B = \frac{5 - 0.7}{200k} = 0.0215\text{ mA}$
- Since  $I_{CO} \ll I_B$ , therefore,  $I_C = \beta I_B = 2.15\text{ mA}$
- From the collector circuit,  $V_{CE} = 10 - 3 \times 2.15 = 3.55\text{ V}$
- Since,  $V_{CE} = V_{CB} + V_{BE}$
- Thus,  $V_{CB} = 3.55 - 0.7 = 2.85\text{ V}$



Find the transistor currents and voltages in the circuit shown in fig. if  $I_{CO} = 20\text{nA}$ ,  $\beta = 100$

$$-10 + (3\text{K})I_C + V_{CE} = 0$$
$$V_{CE} =$$

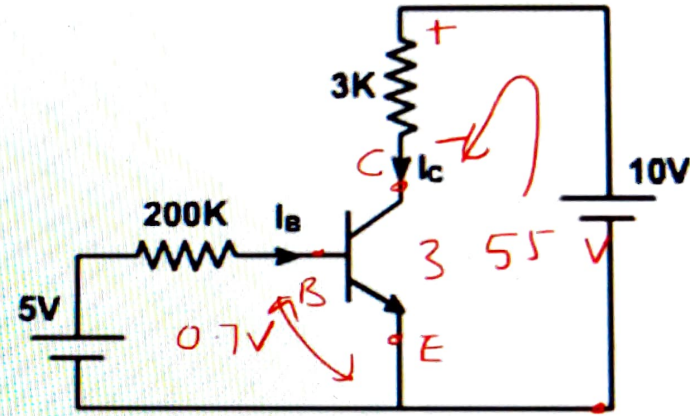- For the base circuit,  $5 = 200 \times I_B + 0.7$
- Therefore,  $I_B = \frac{5-0.7}{200\text{k}} = 0.0215\text{mA}$
- Since  $I_{CO} \ll I_B$ , therefore,  $I_C = \beta I_B = 2.15\text{mA}$
- From the collector circuit,  $V_{CE} = 10 - 3 \times 2.15 = \underline{\underline{3.55\text{V}}}$
- Since,  $V_{CE} = V_{CB} + V_{BE}$
- Thus,  $V_{CB} = 3.55 - 0.7 = \underline{\underline{2.85\text{V}}}$



$$V_{CE} = \underline{\underline{V_{CB} + V_{BE}}}$$



$$\beta = 100$$

